

## Lecture 24 - Intrin. Freq. Limits - Outline

- **Announcements**

Final Exam - Tuesday, Dec 15, 9:00 am - 12 noon

- **Review - Shunt feedback capacitances:**  $C_{\mu}$  and  $C_{gd}$

**Miller effect:** any C bridging a gain stage looks bigger at the input

**Marvelous cascode:** CE/S-CB/G (E/SF-CB/G work, too - see  $\mu A741$ )

large bandwidth, large output resistance

used in gain stages and in current sources

**Using the Miller effect to advantage:** Stabilizing OP Amps - the  $\mu A741$

- **Intrinsic high frequency limitations of transistors**

**General approach**

**MOSFETs:**  $f_T$

biasing for speed

impact of velocity saturation


design lessons

**BJTs:**  $f_{\beta}$ ,  $f_T$ ,  $f_{\alpha}$

biasing for speed

design lessons


## Summary of OCTC and SCTC results

 

- **OCTC**: an estimate for  $\omega_{HI}$ 
  1.  $\omega_{HI}^*$  is a weighted sum of  $\omega$ 's associated with device capacitances:  
(add RC's and invert)
  2. Smallest  $\omega$  (largest RC) dominates  $\omega_{HI}^*$
  3. Provides a lower bound on  $\omega_{HI}$
- **SCTC**: an estimate for  $\omega_{LO}$ 
  1.  $\omega_{LO}^*$  is a weighted sum of  $\omega$ 's associated with bias capacitors:  
(add  $\omega$ 's directly)
  2. Largest  $\omega$  (smallest RC) dominates  $\omega_{LO}^*$
  3. Provides an upper bound on  $\omega_{LO}$

 
## The Miller effect (general)

Consider an amplifier shunted by a capacitor, and consider how the capacitor looks at the input and output terminals:




$$i_{in} = C_m \frac{d[(1 - A_v)v_{in}]}{dt} = (1 - A_v)C_m \frac{dv_{in}}{dt}$$

Note:  $A_v$  is negative

 

$C_{in}$  looks much bigger than  $C_m$

 


$C_{out}$  looks like  $C_m$

$$C_m \frac{(1 - A_v)}{A_v} \approx C_m$$
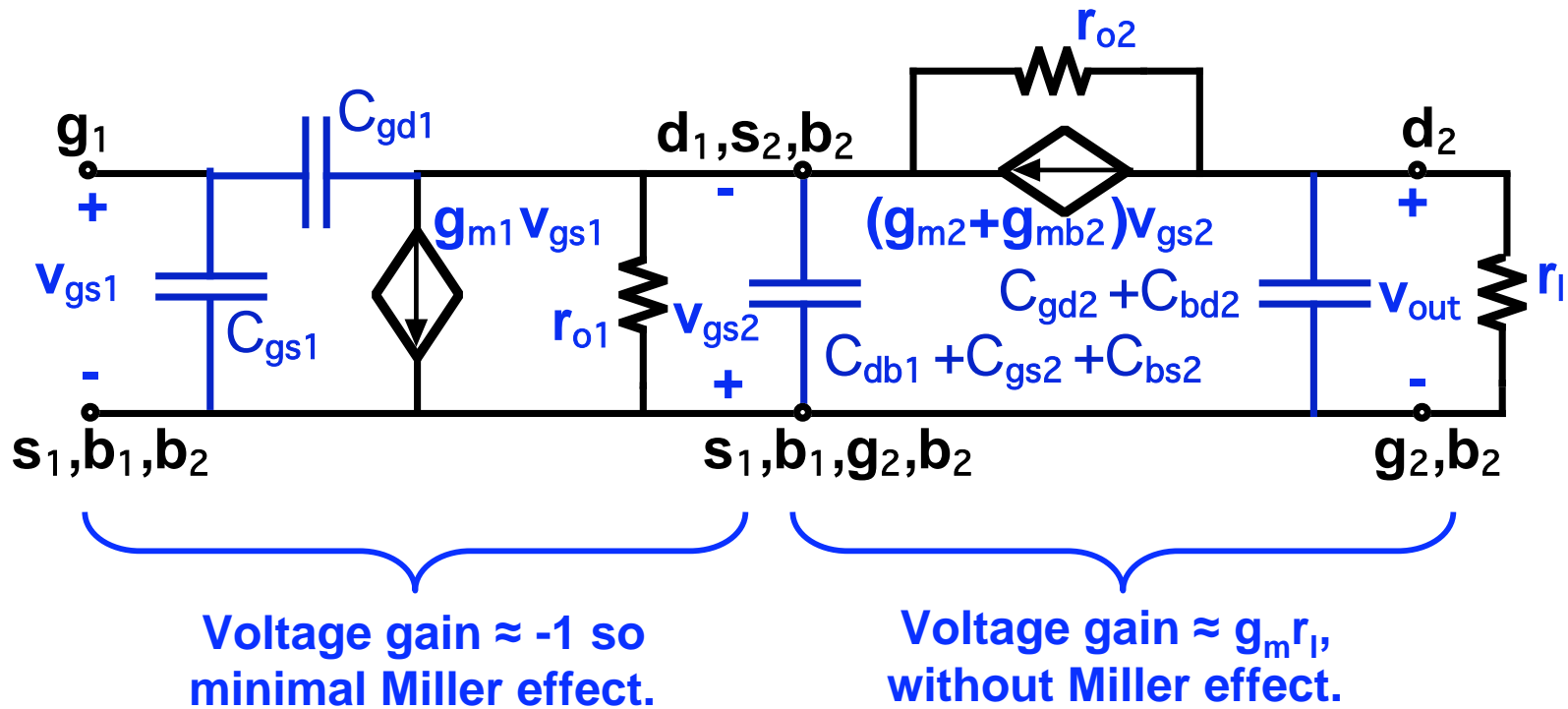
## The cascode when the substrate is grounded:

High frequency issues:

**L.E.C. of cascode:** can't use equivalent transistor idea here because it didn't address the issue of the C's!




Common-source gain without the Miller effect penalty!
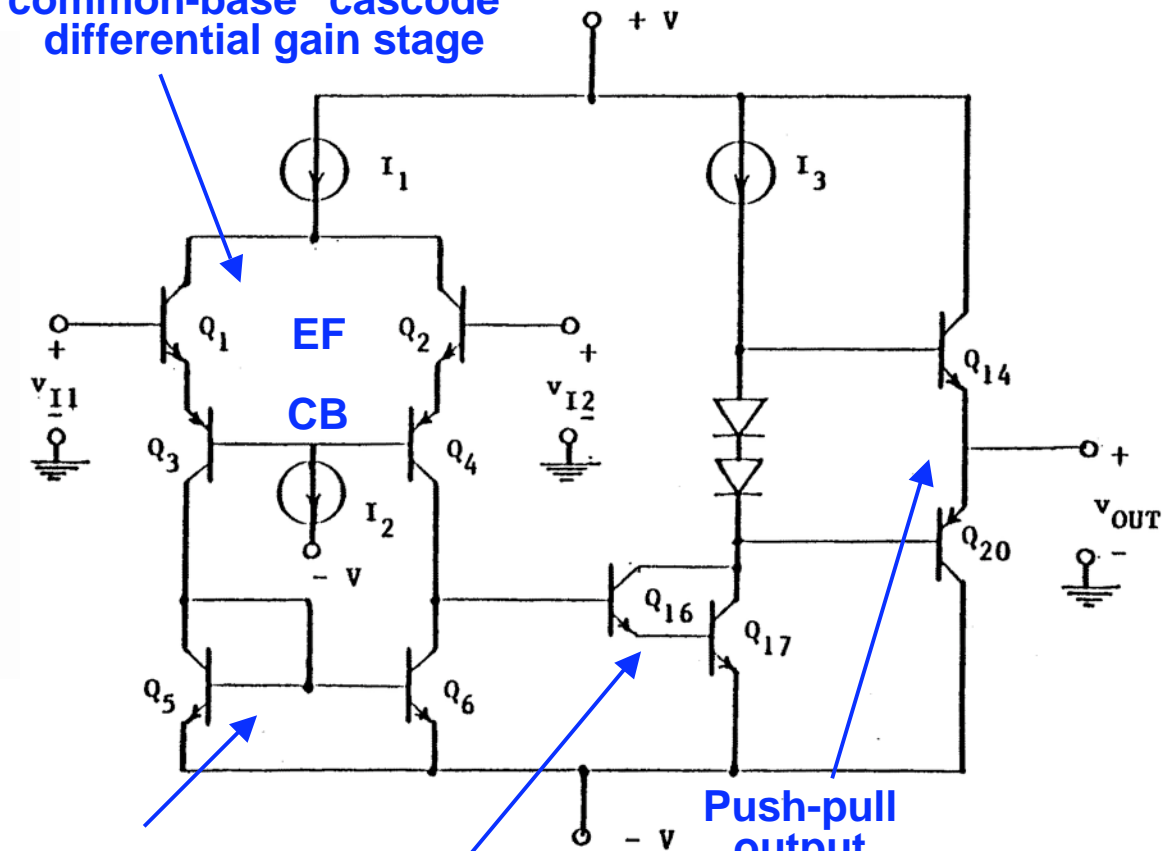
# Multi-stage amplifier analysis and design: The $\mu A741$

Figuring the circuit out:

Emitter-follower/  
common-base "cascode"  
differential gain stage




Push-pull  
output

Simplified schematic

Darlington common-emitter  
gain stage

Current mirror load





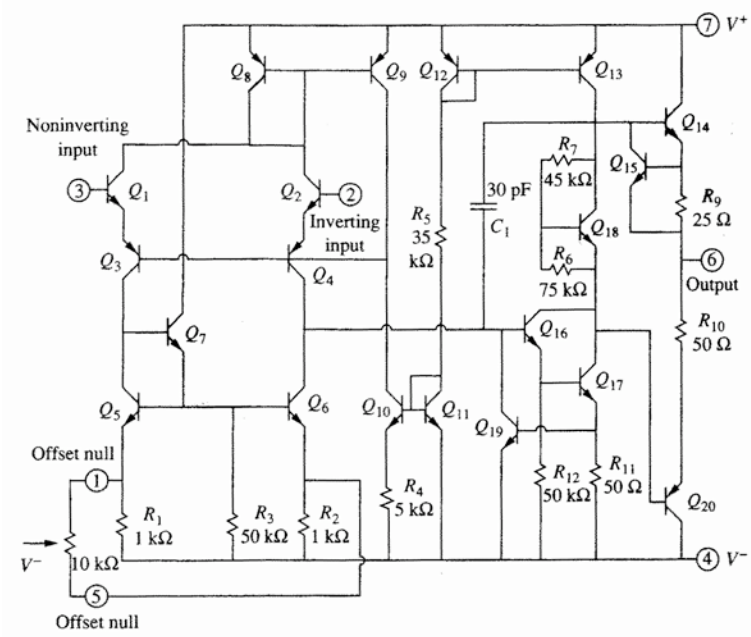


The full schematic

© Source unknown. All rights reserved.  
This content is excluded from our Creative Commons license.  
For more information, see <http://ocw.mit.edu/fairuse>.
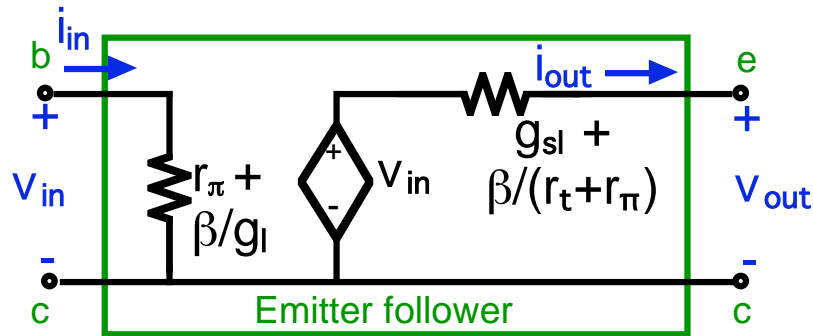   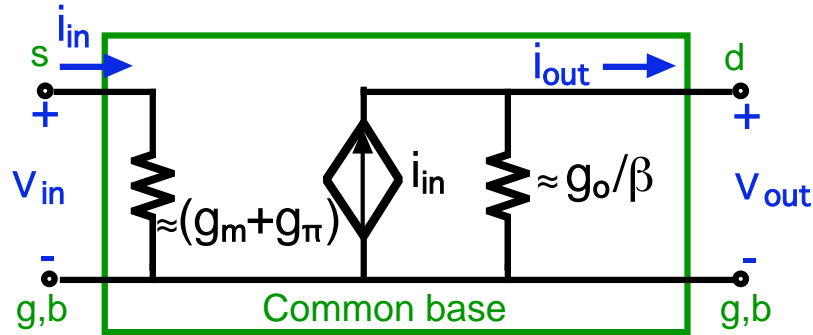
# Multi-stage amplifier analysis and design: Understanding the $\mu$ A741 input "cascode"

Begin with the BJT building-block stages:






### Relative sizes:

- $g_m$ : large
- $g_\pi$ : medium
- $g_o$ : small
- $g_t, g_i$ : cannot generalize
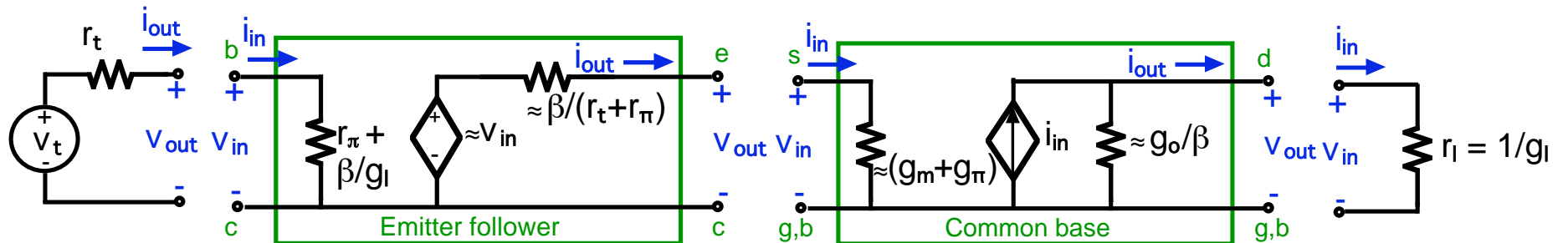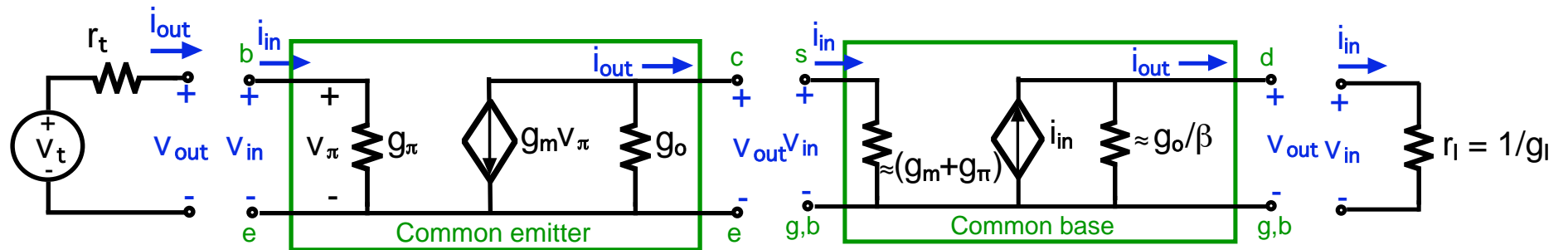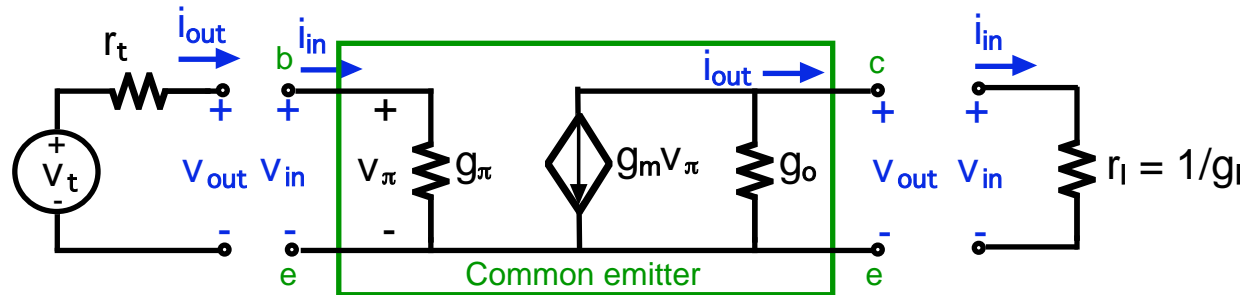
# Multi-stage amplifier analysis and design: Two-port models






Two different "cascode" configurations, this time bipolar:



In a bipolar cascode, starting with an emitter follower still reduces the gain, but it also gives twice the input resistance, which is helpful.

# Multi-stage amplifier analysis and design: MOSFET 2-port models

Reviewing our building-block stages:

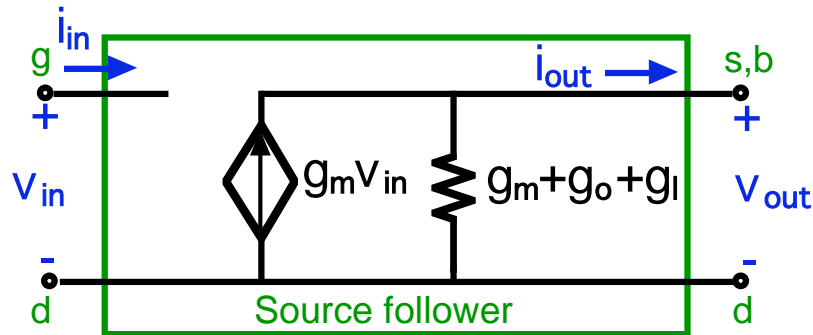  
 
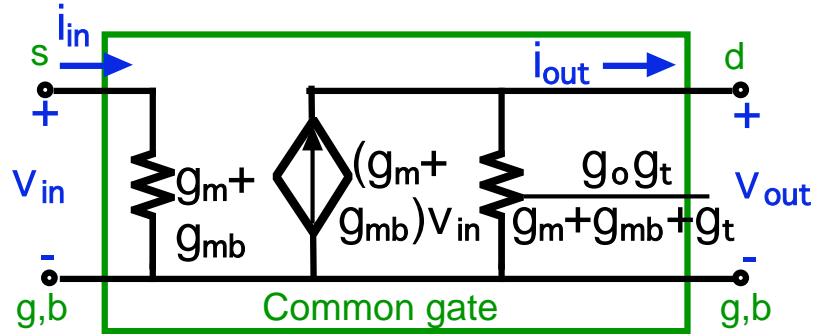


**Relative sizes:**  
 $g_m, g_{mb}$ : large  
 $g_o$ : small  
 $g_t, g_l$ : cannot generalize



# Multi-stage amplifier analysis and design: Two-port models

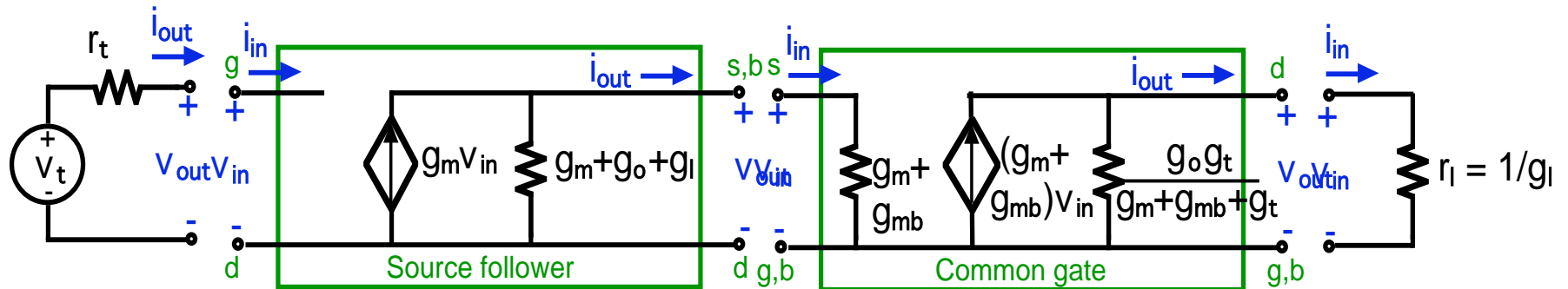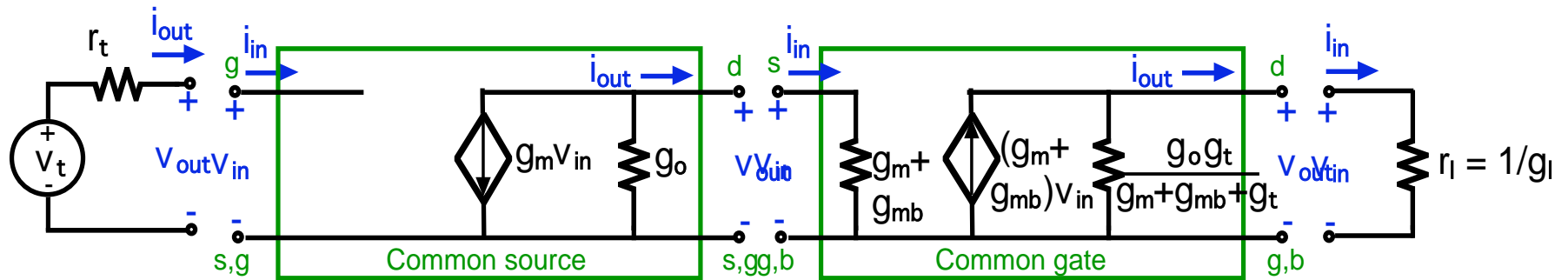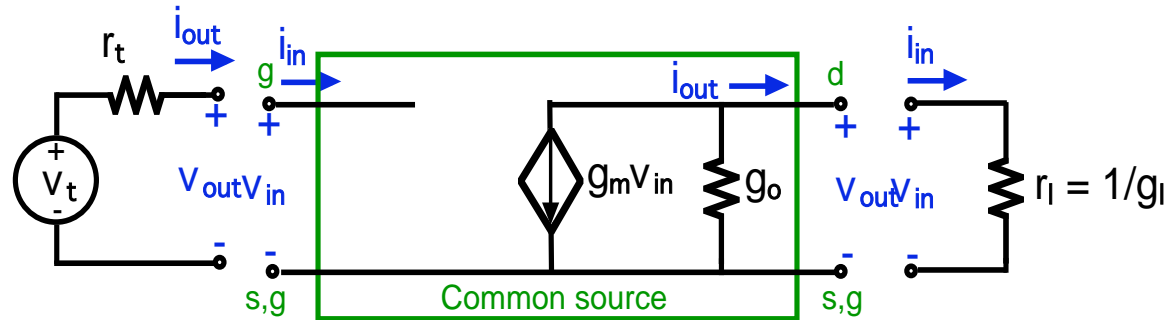
## Two different "cascode" configurations:



With MOSFETs, starting a cascode with a source follower costs a factor of two in gain because  $r_{out}$  for an SF is small, so it isn't very attractive.

# Multi-stage amplifier analysis and design: The $\mu\text{A741}$

The circuit: a full schematic

 


$C_1$  is in a Miller position across  $Q_{16}$

The monolithic capacitor made the  $\mu\text{A741}$  "complete" and a big success. Why is it needed? What does it do?
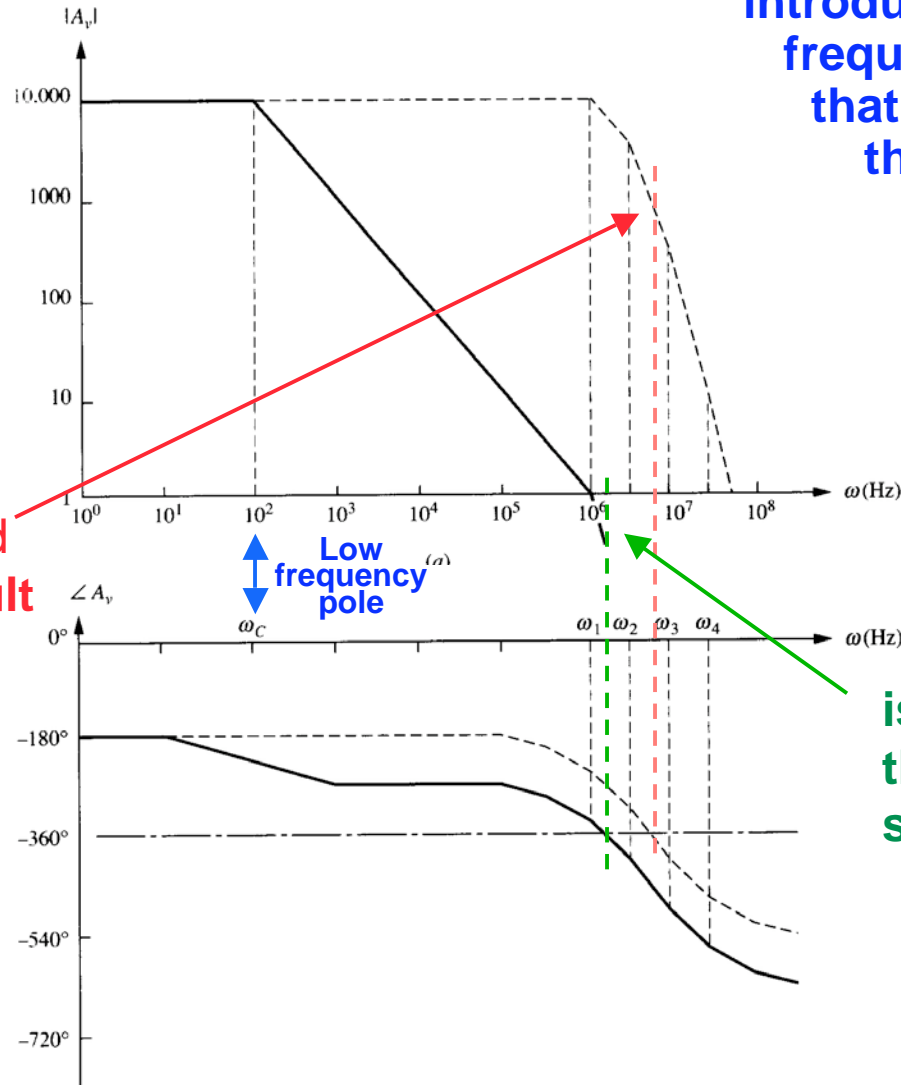
# Multi-stage amplifier analysis and design: The $\mu\text{A}741$

Why is there a capacitor in the circuit?: the added capacitor introduces a low frequency pole that stabilizes the circuit.

Without it the gain is still greater than 1 when the phase shift exceeds  $180^\circ$  (dashed curve). This can result in positive feedback and instability.




introduces a low frequency pole that stabilizes the circuit.

With it the gain is less than 1 by the time the phase shift exceeds  $180^\circ$  (solid curve).

## Intrinsic performance - the best we can do

We've focused on  $\omega_{HI}$ , the upper limit of mid-band, but even when  $\omega > \omega_{HI}$  the  $|A_v| > 1$ , and the circuit is useful. For example, for the common source stage we had

 
$$A_v(j\omega) = \frac{-g_t(g_m - j\omega C_{gd})}{\{(j\omega)^2 C_{gs} C_{gd} + j\omega[(g_l + g_o)C_{gs} + (g_l + g_o + g_t + g_m)C_{gd}] + (g_l + g_o)g_t\}}$$




When we look for a metric to compare the ultimate performance limits of transistors, we make note of this and ask how high can a device in isolation have provide voltage or current gain?
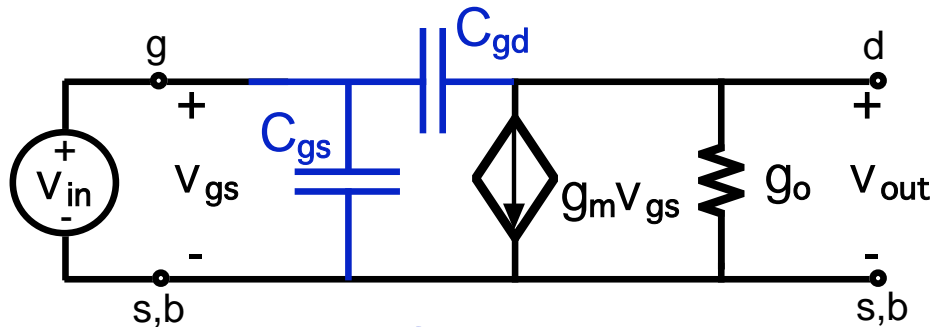
## Intrinsic performance - the best we can do, cont.

Consider the two possibilities shown below, one for a voltage input and output where the metric would be the open circuit voltage gain,  $A_{v,oc}$ , and the other for a current input and output with the metric being the short circuit current gain,  $A_{i,sc}$  (commonly written  $\beta_{sc}$ ):



 
$$A_{v,oc}(s) \equiv \frac{v_{out}(j\omega)}{v_{in}(j\omega)} = - \frac{g_m - j\omega C_{gd}}{g_o - j\omega C_{gd}}$$



$$\beta_{sc}(j\omega) \equiv \frac{i_d(j\omega)}{i_g(j\omega)} = \frac{g_m - j\omega C_{gd}}{j\omega(C_{gs} + C_{gd})}$$

Of these two alternatives,  $\beta_{sc}$  is the more useful.  $A_{v,oc}$  is derived with a voltage source driving a capacitor, something that doesn't give a meaningful result and leads to ever increasing input power. It also does not involve  $g_m$  and  $C_{gs}$ . Consequently, short circuit current gain is used as the intrinsic high frequency performance metric for transistors.
 
## Intrinsic $\omega_{HI}$ 's for MOSFETs - short-circuit current gain



The common-source short-circuit current gain is:


$$\beta_{sc}(j\omega) \equiv \frac{i_d(j\omega)}{i_g(j\omega)} = \frac{g_m - j\omega C_{gd}}{j\omega(C_{gs} + C_{gd})}$$

there is one pole at  $\omega = 0$ , and one zero,  $\omega_z$ :

$$\omega_z = \frac{g_m}{C_{gd}}$$

The short circuit current gain,  $\beta_{sc}$ , is infinite at DC ( $\omega = 0$ ), and its magnitude decreases linearly with increasing frequency.
 
## Intrinsic $\omega_{HI}$ 's for MOSFETs - short-circuit current gain, cont.




The magnitude of  $\beta_{sc}$  decreases with  $\omega$ , but it is still greater than one for a wide range of frequencies.

$$|\beta_{sc}(j\omega)| = \sqrt{\frac{g_m^2 + \omega^2 C_{gd}^2}{\omega^2 (C_{gs} + C_{gd})^2}}$$

The transistor is useful until  $|\beta_{sc}|$  is less than one. The frequency at which this occurs is called  $\omega_t$ . Setting = 1 and solving for  $\omega_t$  yields:


$$\omega_t = \sqrt{\frac{g_m^2}{[(C_{gs} + C_{gd})^2 - C_{gd}^2]}} \approx \frac{g_m}{(C_{gs} + C_{gd})}$$

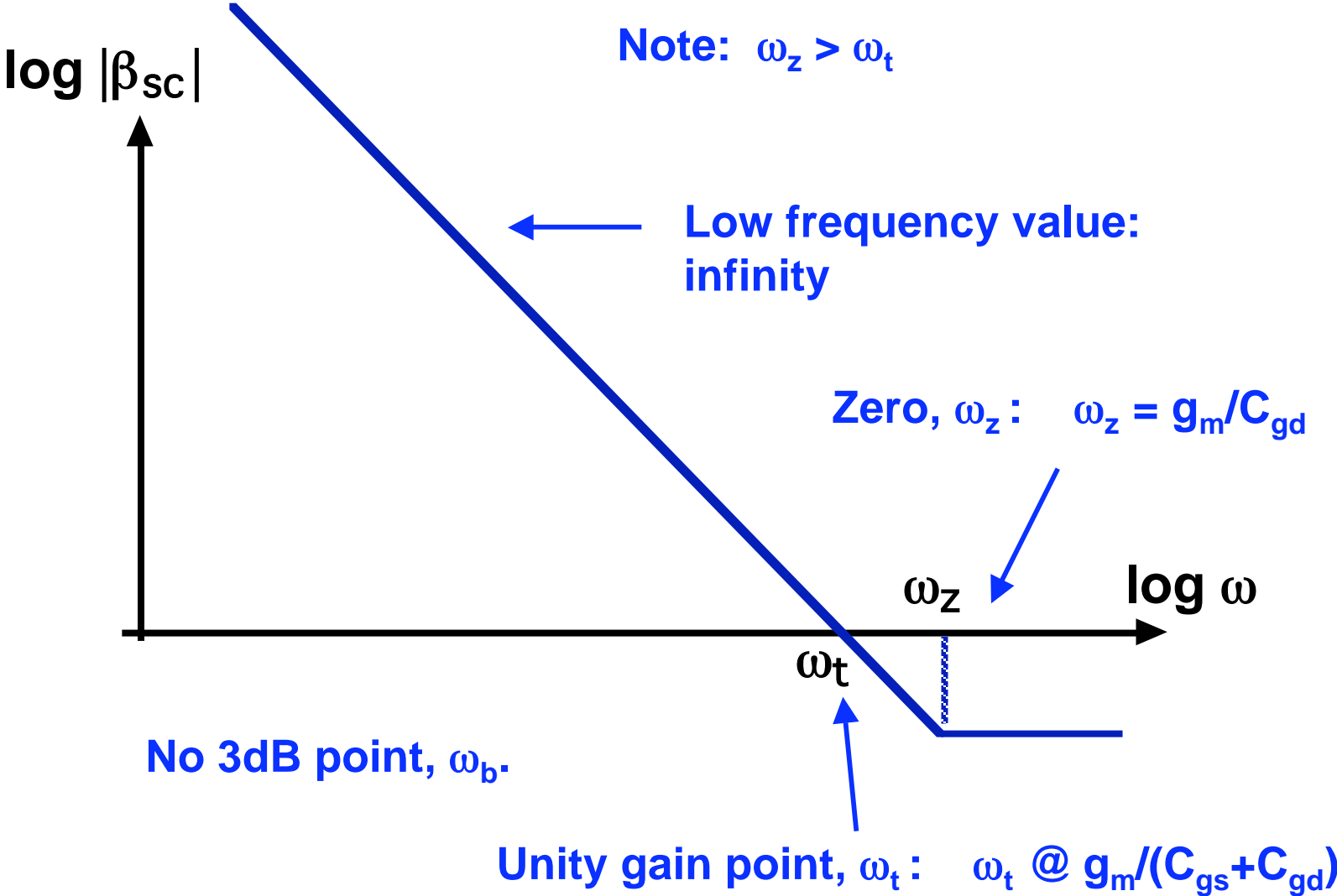MOSFET short-circuit current gain,  $\beta_{sc}(j\omega)$ , cont.




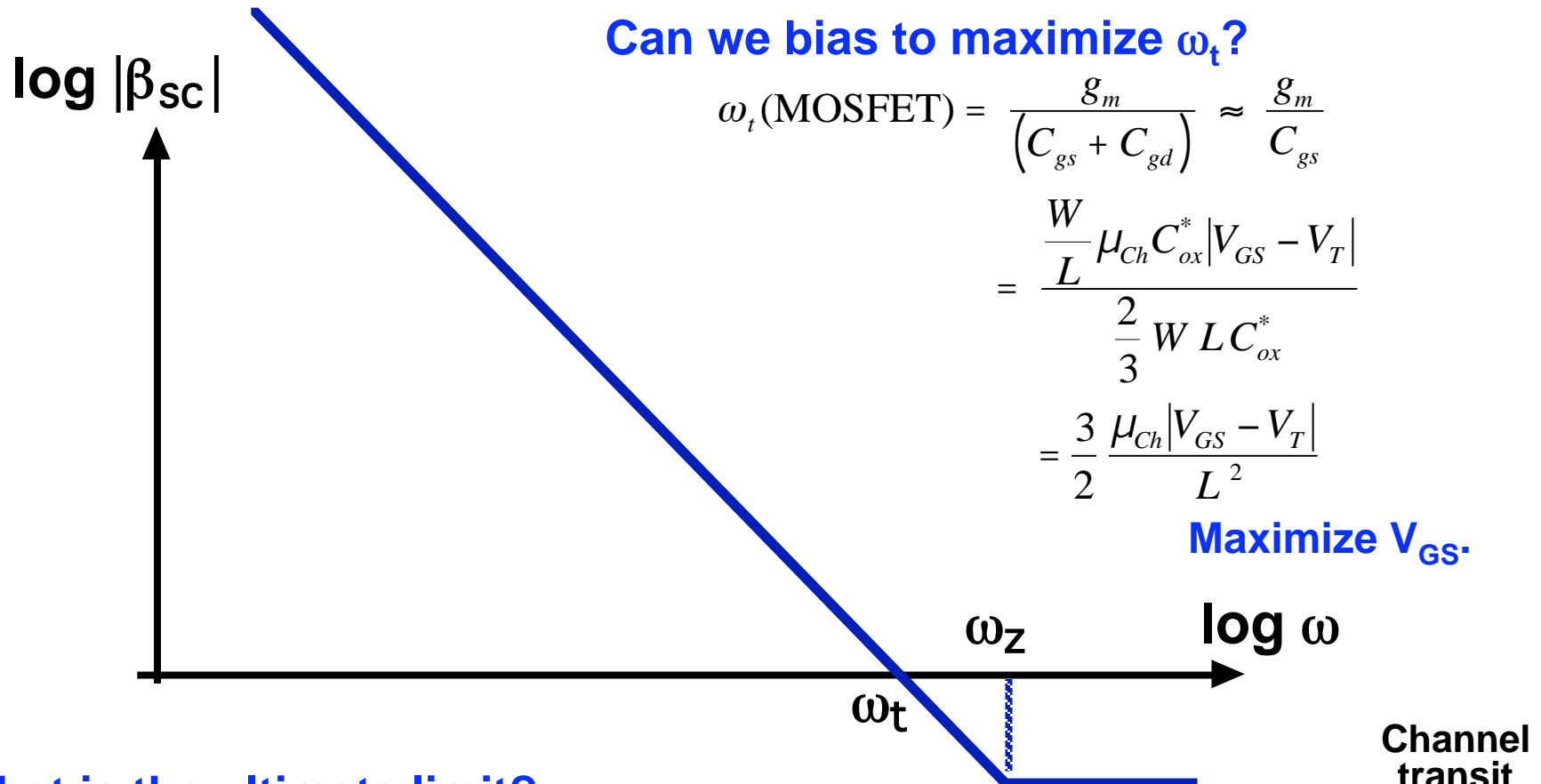
## MOSFET short-circuit current gain, $\beta_{sc}(j\omega)$ , cont.



$$\begin{aligned} \omega_t(\text{MOSFET}) &= \frac{g_m}{(C_{gs} + C_{gd})} \approx \frac{g_m}{C_{gs}} \\ &= \frac{\frac{W}{L} \mu_{Ch} C_{ox}^* |V_{GS} - V_T|}{\frac{2}{3} W L C_{ox}^*} \\ &= \frac{3}{2} \frac{\mu_{Ch} |V_{GS} - V_T|}{L^2} \end{aligned}$$

**Maximize  $V_{GS}$ .**

**What is the ultimate limit?**

$$\omega_t(\text{MOSFET}) = \frac{3}{2} \frac{\mu_{Ch} |V_{GS} - V_T|}{L^2} = \frac{3}{2L} \mu_{Ch} \frac{|V_{DS}|}{L} = \frac{3}{2L} \mu_{Ch} \overline{E_{Ch}} = \frac{3}{2} \frac{\overline{s_{Ch}}}{L} = \frac{1}{\tau_{Ch}}$$

**Channel transit time!**

**Lessons: Bias at well above  $V_T$ ; make  $L$  small, use n-channel.**

An aside: looking back at CMOS gate delays

**CMOS:** switching speed; minimum cycle time (from Lec. 15)

Gate delay/minimum cycle time:

For MOSFETs operating in strong inversion, no velocity saturation:

$$\tau_{Min\ Cycle} = \frac{12nL_{min}^2 V_{DD}}{\mu_e [V_{DD} - V_{Tn}]^2}$$

Comparing this to the channel transit time:

$$\tau_{Ch\ Transit} = \frac{L_{min}}{\bar{s}_{e,Ch}} = \frac{L_{min}}{\mu_e E_{Ch}} = \frac{L_{min}}{\mu_e (V_{DD} - V_{Tn})/L_{min}}$$

We see that the cycle time is a multiple of the transit time:

$$\tau_{Min\ Cycle} = \frac{12nV_{DD}}{(V_{DD} - V_{Tn})} \tau_{Channel\ Transit} = n' \tau_{Channel\ Transit}$$

When velocity saturation dominated, we found the same thing:

$$\tau_{Min.Cycle} \propto \frac{L_{min} V_{DD}}{s_{sat} [V_{DD} - V_{Tn}]} = n' \tau_{ChanTransit} \quad \text{where} \quad \tau_{ChanTransit} = \frac{L}{s_{sat}}$$

## Intrinsic $\omega_{HI}$ 's for MOSFETs - $\beta_{sc}(j\omega)$ and $\omega_t$ w. velocity saturation

What about the intrinsic  $\omega_{HI}$  of a MOSFET operating with full velocity saturation?

The basic result is unchanged; we still have:

$$\omega_t = \sqrt{\frac{g_m^2}{[(C_{gs} + C_{gd})^2 - C_{gd}^2]}} \approx \frac{g_m}{(C_{gs} + C_{gd})} \approx \frac{g_m}{C_{gs}}$$

However, now  $g_m$  is different:

$$g_m = W s_{sat} C_{ox}^*$$


With this we have:

$$\omega_t \approx \frac{g_m}{C_{gs}} = \frac{W s_{sat} C_{ox}^*}{W L C_{ox}^*} = \frac{s_{sat}}{L} = \frac{1}{\tau_{Ch}}$$

In the case where velocity saturation dominates, we once again find that it is the channel transit time that is the ultimate limit.

Do you care to speculate on the intrinsic  $\omega_{HI}$  of a BJT?
 
## Intrinsic $\omega_{HI}$ 's for BJTs - short-circuit current gain



The common-emitter short-circuit current gain is:

$$\beta_{sc}(j\omega) \equiv \frac{i_c(j\omega)}{i_b(j\omega)} = \frac{g_m - j\omega C_\mu}{[g_\pi + j\omega(C_\pi + C_\mu)]}$$


there is one pole, call it  $\omega_p$ , and one zero,  $\omega_z$ :

$$\omega_p = \frac{g_\pi}{(C_\pi + C_\mu)}, \quad \omega_z = \frac{g_m}{C_\mu}$$

Of these two,  $\omega_p$  is much smaller and this is the 3dB point of the common-emitter short-circuit current gain. We give it the name  $\omega_\beta$ :

$$\omega_\beta = \frac{g_\pi}{(C_\pi + C_\mu)}$$
 
## Intrinsic $\omega_{HI}$ 's for BJTs - short-circuit current gain, cont.



The magnitude of  $\beta_{sc}$  decreases above  $\omega_b$ , but it is still greater than one initially:


$$|\beta_{sc}(j\omega)| = \sqrt{\frac{g_m^2 + \omega^2 C_\mu^2}{[g_\pi^2 + \omega^2 (C_\pi + C_\mu)^2]}}$$

The transistor is useful until  $|\beta_{sc}|$  is less than one. The frequency at which this occurs is called  $\omega_t$ . Setting = 1 and solving for  $\omega_t$  yields:


$$\omega_t = \sqrt{\frac{(g_\pi^2 + g_m^2)}{[(C_\pi + C_\mu)^2 - C_\mu^2]}} \approx \frac{g_m}{(C_\pi + C_\mu)}$$
 
## BJT short-circuit current gain, $\beta_{sc}(j\omega)$ , cont.

Note:  $\omega_z > \omega_t \gg \omega_\beta (= \omega_t/\beta_F)$


 
## BJT short-circuit current gain, $\beta_{sc}(j\omega)$ , cont.



In the limit of large  $I_C$ :  $\lim_{I_C \rightarrow \infty} \omega_t \approx \frac{1}{\tau_b} = \frac{2D_{\min,B}}{w_B^2} = \frac{2\mu_{\min,B} V_{thermal}}{w_B^2}$

Base transit time  $\rightarrow \tau_b$

**Lessons: Bias at large  $I_C$ ; make  $w_B$  small, use npn.**

## Lecture 24 - Intrinsic Limits of Transistor Speed - Summary

- **Intrinsic high frequency limits for transistors**

**General approach:** short-circuit current gains

- **Limits for MOSFETs:**

**Metric - CS short-circuit current unity gain pt:**  $\omega_T = g_m / [(C_{gs} + C_{gd})^2 - C_{gd}^2]^{1/2}$

$\omega_T$  is approximately  $g_m / C_{gs} = 3\mu_e (V_{GS} - V_T) / 2L^2$

$g_m = (W/L)\mu_e C_{ox}^* (V_{GS} - V_T)$  and  $C_{gs} = (2/3)WLC_{ox}^*$

so  $\omega_T \approx 3\mu_e (V_{GS} - V_T) / 2L^2 = 1/\tau_{ch}$

**Design lessons:** bias at large  $I_D$

minimize  $L$  (win as  $L^2$ ; as  $L$  in velocity saturation)

use n-channel rather than p-channel ( $\mu_e \gg \mu_h$ )

- **Limits for BJTs:**

**Metrics - CE short-circuit current gain 3B pt:**  $\omega_b = g_p / (C_\pi + C_\mu)$

**CE short-circuit current gain unit gain pt:**  $\omega_T = g_m / (C_\pi + C_\mu)$

$\omega_T$  approaches  $1/\tau_b$  as  $I_c$  increases and  $\tau_b = w_B^2 / 2D_{min,B}$

so  $\omega_T \approx 2D_{min,B} / w_B^2 = 2\mu_e V_t / w_B^2 = 1/\tau_b$

**CB short-circuit current gain unit gain pt:**  $\omega_\alpha = g_m / C_\pi$

**Design lessons:** bias at high collector current

minimize  $w_B$  (win as  $w_B^2$ )

use npn rather than pnp ( $\mu_e \gg \mu_h$ )



MIT OpenCourseWare  
<http://ocw.mit.edu>

6.012 Microelectronic Devices and Circuits  
Fall 2009

For information about citing these materials or our Terms of Use, visit: <http://ocw.mit.edu/terms>.