

Massachusetts Institute of Technology
Department of Nuclear Science and Engineering
Department of Electrical Engineering and Computer Science


22.071/6.071 - Introduction to Electronics, Signals and Measurement
Spring 2006

Homework 10
 Due 5/3/06

Problem 1.


For the following circuit:

Calculate the voltages V_N , V_P and V_O

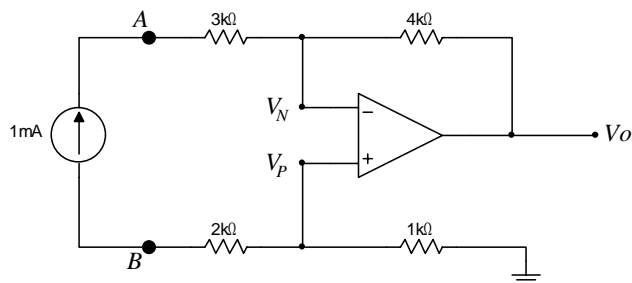


Problem 2.

For these circuits calculate the gain and the input resistance seen by the input signal V_i . Assume ideal op-amps.

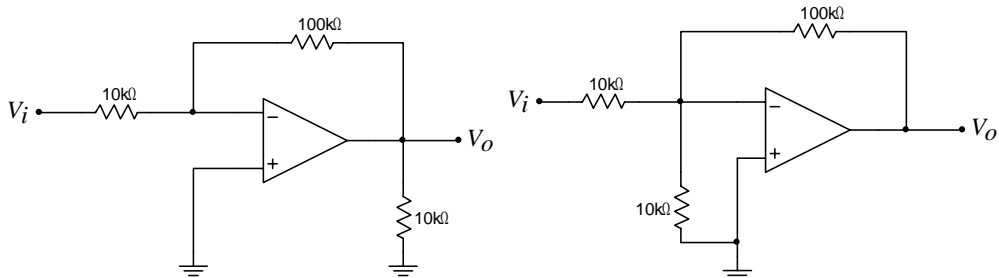


Problem 3.

Calculate the gain $A = \frac{V_o}{V_i}$ for the following ideal op-amp circuit

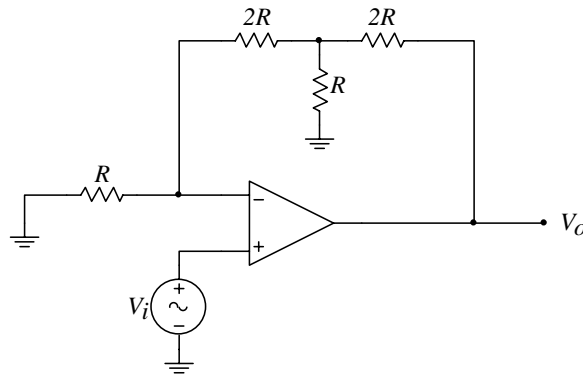

Problem 4.

The op-amp in the following circuit outputs a current of 5 mA. ($I_o = 5$ mA). The transistor has $\beta = 100$. Calculate the value of the resistor R .

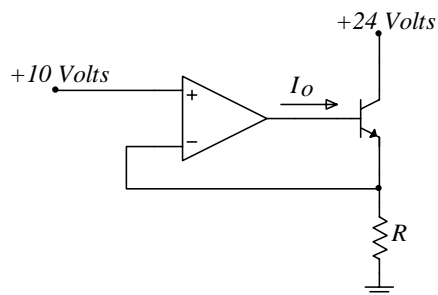

Problem 5.

The following circuit is a high pass filter.

1. Derive the voltage transfer function V_o/V_i
2. What is the voltage gain at low and at high frequencies?
3. At what frequency is the magnitude of the gain $1/\sqrt{2}$ of the maximum value?

