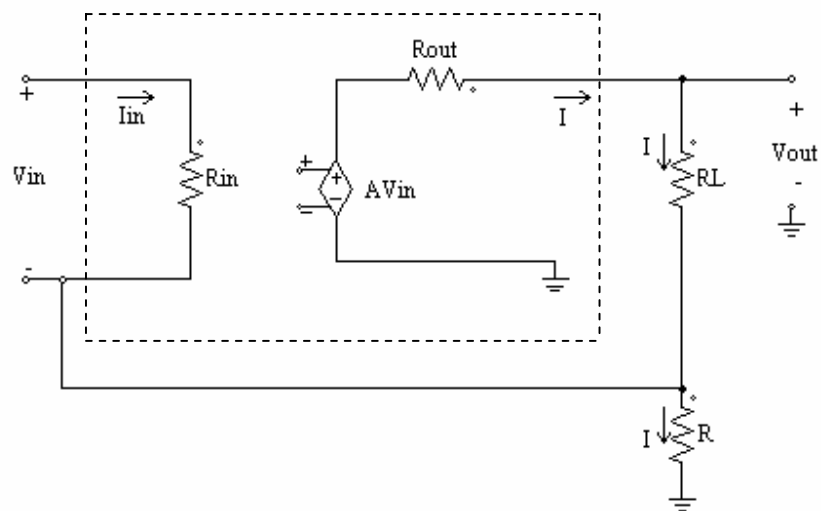


MASSACHUSETTS INSTITUTE OF TECHNOLOGY
22.071/6.071 Introduction to Electronics, Signals and Measurement
Spring 2006

Laboratory 9: Dependent sources, Op-Amps, Current Source.


We have been introduced to dependent sources and have analyzed the following circuit.



The dependent source in the above circuit is a voltage controlled voltage source whose output is proportional to V_{in} with a constant of proportionality $A \gg 1$. Additionally we know that resistance R_{in} is large ($M\Omega$ in practical devices) and resistance R_{out} is small ($10s \Omega$).

The large value of the resistance R_{in} implies that the amount of current flowing through R_{in} is very small (zero in the ideal case). If we assume that the input voltage V_{in} corresponds to an output of a transducer then we see that this circuit does not demand the delivery of power from the sensor circuit. In other words our transducer device, whose goal is to just give an electrical signal that is related to some physical quantity, is buffered (protected, isolated) from the demands of the measuring circuit.

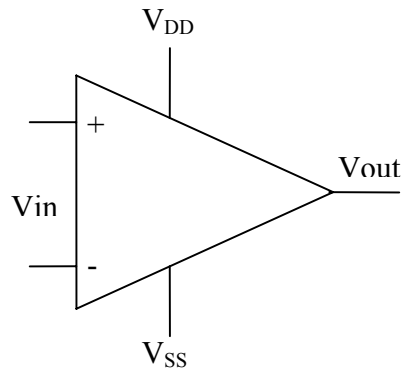
The part of the circuit enclosed by the dashed lines is a device called the Operational Amplifier (op-amp). The schematic of an op-amp is:



The terminals labeled VDD and VSS are the positive and negative power supply connections for the device.

In this class we will use the LF356 op amp. The 356 is a good, cheap, easy to work with op amp well suited to most basic circuits. More expensive op amps tend to sacrifice op-amp ideality (finite input current, stability, power supply reject, etc.) for specific purposes (high speed, low noise etc.) and can be much more difficult to work with. The data sheet for the 356 is available in the class web site.

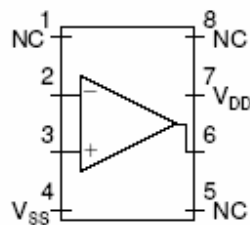
The pinout of the 356 is the same as that of another widely used op amp, the 741, and is shown below.



We will use this op-amp to construct and characterize a **current source**.

Current Source and Power Transfer.

Let's investigate the following circuit.

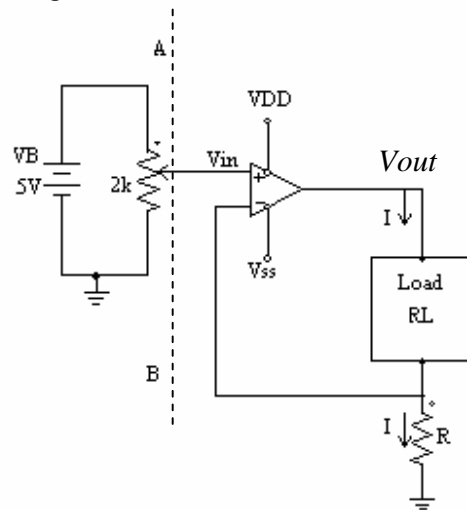


As you recall from the class notes, $V_{out} = V_{in} \frac{R + R_L}{R}$ and the current through resistor R_L is

$$I = \frac{V_{in}}{R}$$

Notice that the current I provided by this circuit does not depend on the value of the resistor R_L , the load resistor. The amount of current flowing through the load is determined by the value of resistor R and the input voltage V_{in} .

Build the circuit shown above. The circuit to the left of the vertical line AB provides the input voltage V_{in} for your current source. For the voltages V_{DD} and V_{SS} use +15V and -15V respectively.

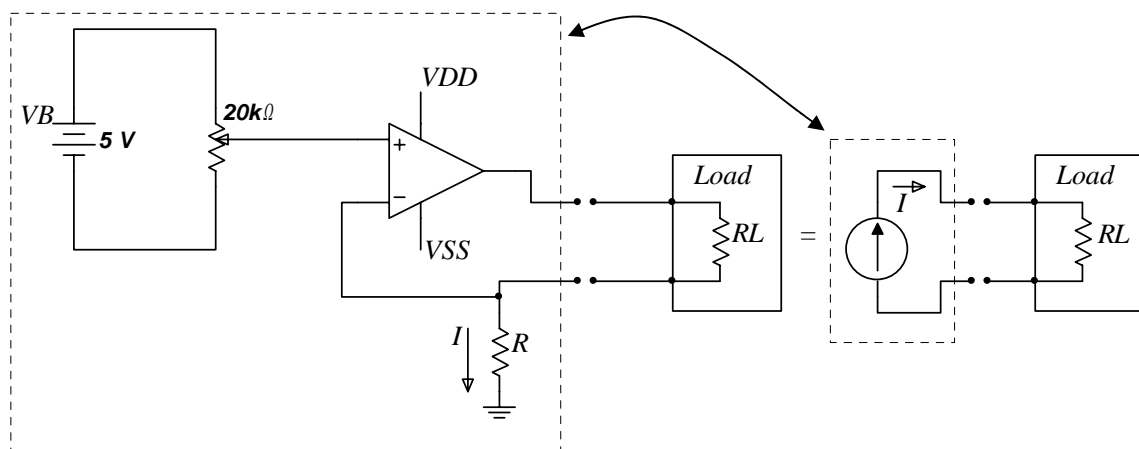You have just built a fundamental current source as indicated below.




Perform the appropriate measurements/calculations and complete the table below.

V_{in}	R_L	R	V_{out} (measured)	I (calculated)	I (measured)
1	1k	1k			
1	10k	1k			
5	1k	1k			
5	1k	10k			
5	10k	1k			


Now that we have constructed a current source let's use it to investigate the simple current divider and related power transfer issues.

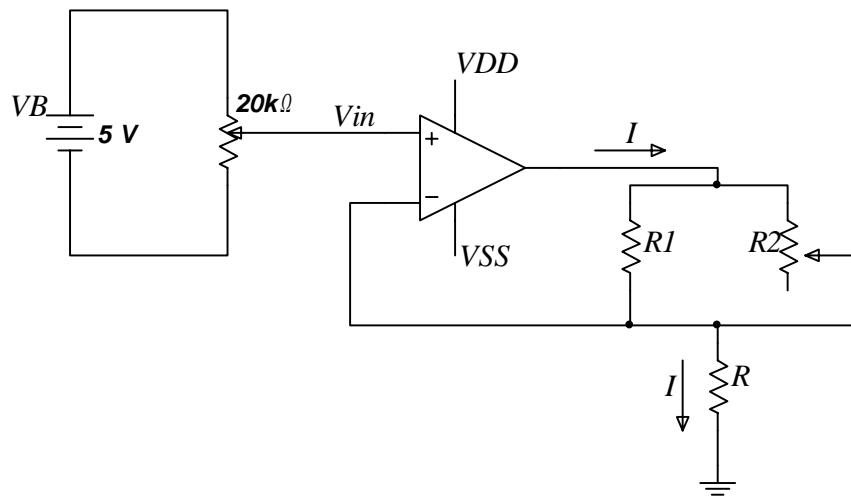We will simply replace the load resistor R_L with two resistors connected in parallel as shown on the circuit below. One of these resistors (R_2) is the variable $20k\Omega$ resistor. For R_1 use a resistor in the range $1k\Omega$ to $10k\Omega$.



Select appropriate values for all relevant circuit parameters in order to generate a current of 10mA. List the parameters and their values.

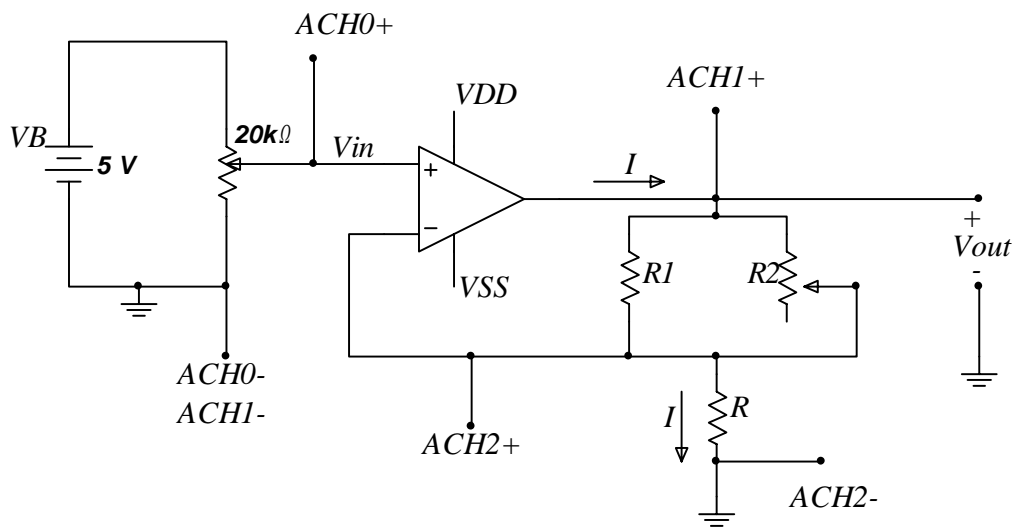Next, let's make the connections indicated in the schematic shown below.



The channel ACH2 measures the current I , while ACH0 and ACH1 measure the voltage V_{in} and V_{out} respectively.

From the class web site download and open the virtual instrument **Current_Divider_01**.


Vary the value of resistance R_2 by trimming the potentiometer. Plot and comment on the power dissipation characteristics of the current divider.

Answer the following:

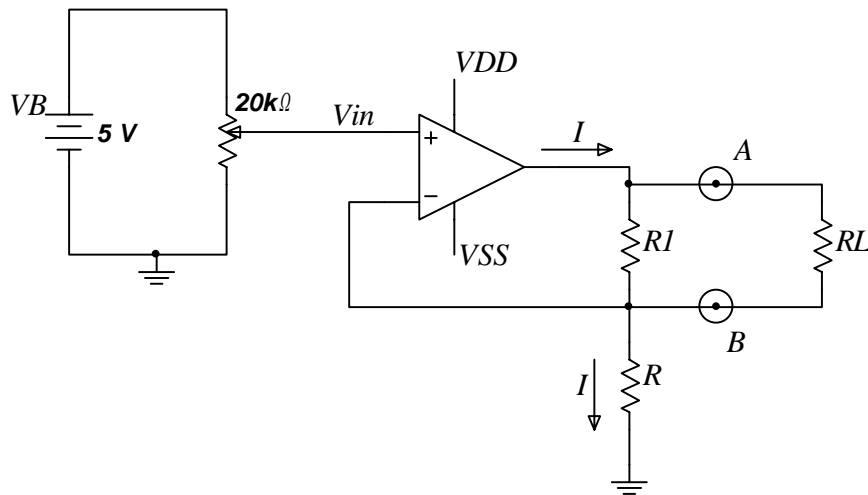
1. Give expressions for the current through resistors R1 and R2
2. Give expressions for the power dissipated in resistors R1 and R2
3. From your experimental results you should observe that as $R_2 \rightarrow 0$, the power dissipated in R1 (P_{R_1}) and the power dissipated in R2 (P_{R_2}), $\rightarrow 0$. Explain this result.
4. Why is there a maximum in P_{R_2} but not in P_{R_1} ?

Equivalent Circuit. – for extra credit -

We will next perform a set of simple measurements in order to determine the Thevenin equivalent circuit seen by resistor R_L .



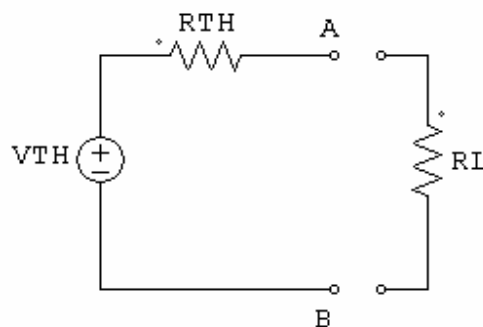In order to determine the Thevenin equivalent circuit we must calculate/measure the equivalent resistance R_{TH} and the equivalent voltage V_{TH} . The resulting equivalent circuit across terminals A and B will have the form:




V_{TH} is the open circuit voltage across terminals AB and R_{TH} , the equivalent resistance, is the ratio of V_{TH} to the short circuit current, I_{SC} , through AB (the Norton current).


$$R_{TH} = \frac{V_{TH}}{I_{SC}}$$

You are free to use any values for the resistors R_1 and R provided that you do not violate the specifications of the operational amplifier.

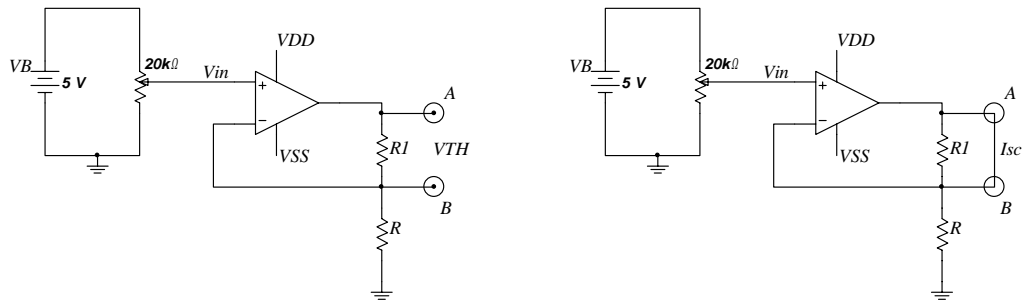Schematically, the measurements are performed as indicated below.



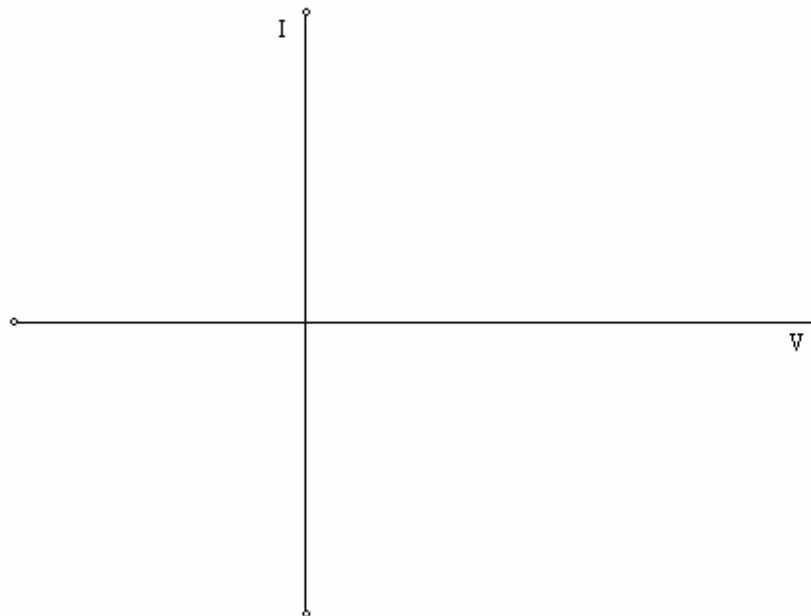Draw a graph of the IV characteristic curve of your equivalent circuit.



Indicate the values of I_{SC} and V_{TH} on the above graph.
Determine the operating point for

$R_L = 1\text{k}\Omega$.

$R_L = 10\text{k}\Omega$.