



The World Leader in High-Performance Signal Processing Solutions

RF Power Amplifiers

May 7, 2003



Outline

- ◆ **PA Introduction**
 - **Power transfer characteristics**
 - **Intrinsic PA metrics**
 - **Linear and Non-linear amplifiers**
 - **PA Architectures**
- ◆ **Single-Stage Linear PA**
 - **Load-line theory**
 - **Transistors size**
 - **Input and Output Matching**
 - **So why is this so hard?**
- ◆ **High-efficiency PAs**
 - **Class A, AB, B and C amplifiers**




Outline (cont.)

- ◆ **Real-World Design Example**
 - **Selecting architecture, number of stages**
 - **Designing stages**
 - **Tuning: inter-stage match and output**
- ◆ **System specifications**
 - **Ruggedness: load mis-match and VSWR**
 - **Linearity: spectral mask (ACPR), switching transients**
 - **Noise in receive band**
- ◆ **Power Control**



PA Transfer characteristics


Defining linearity:

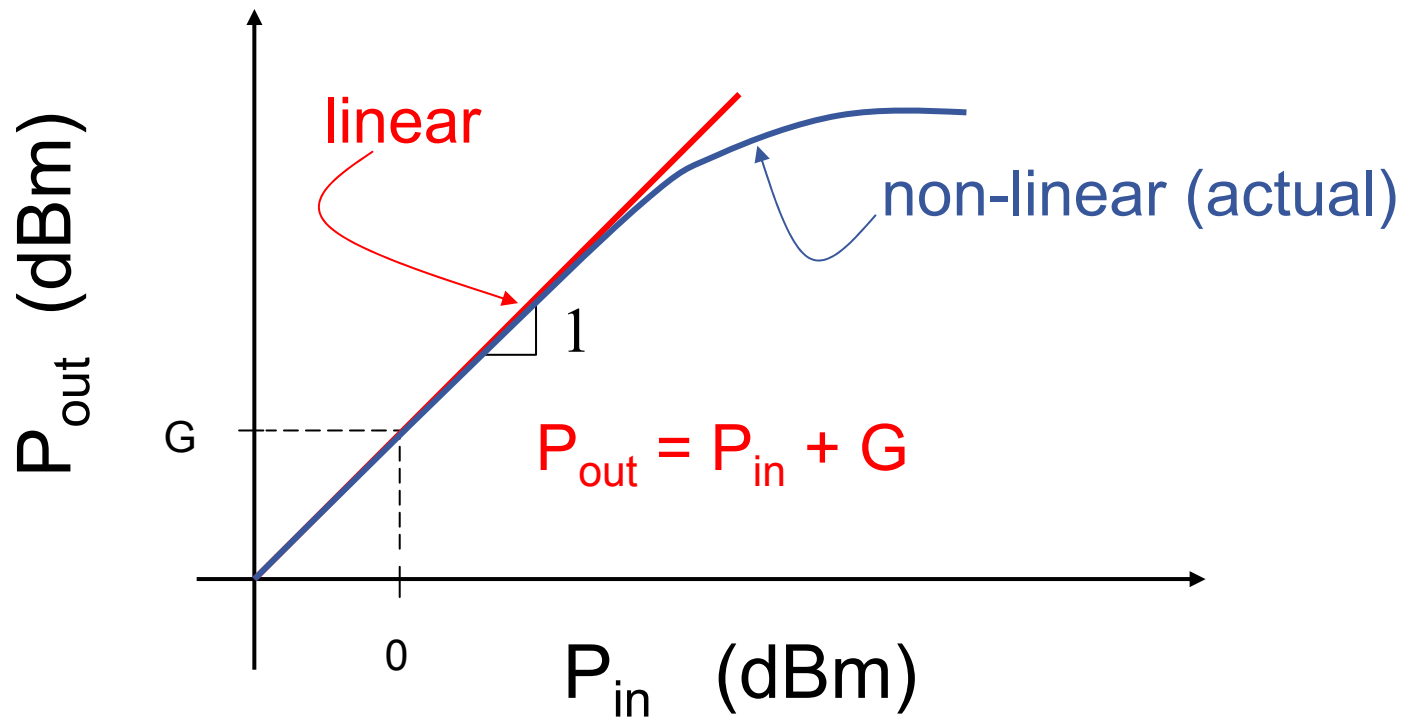



PA Transfer characteristics

Defining linearity:

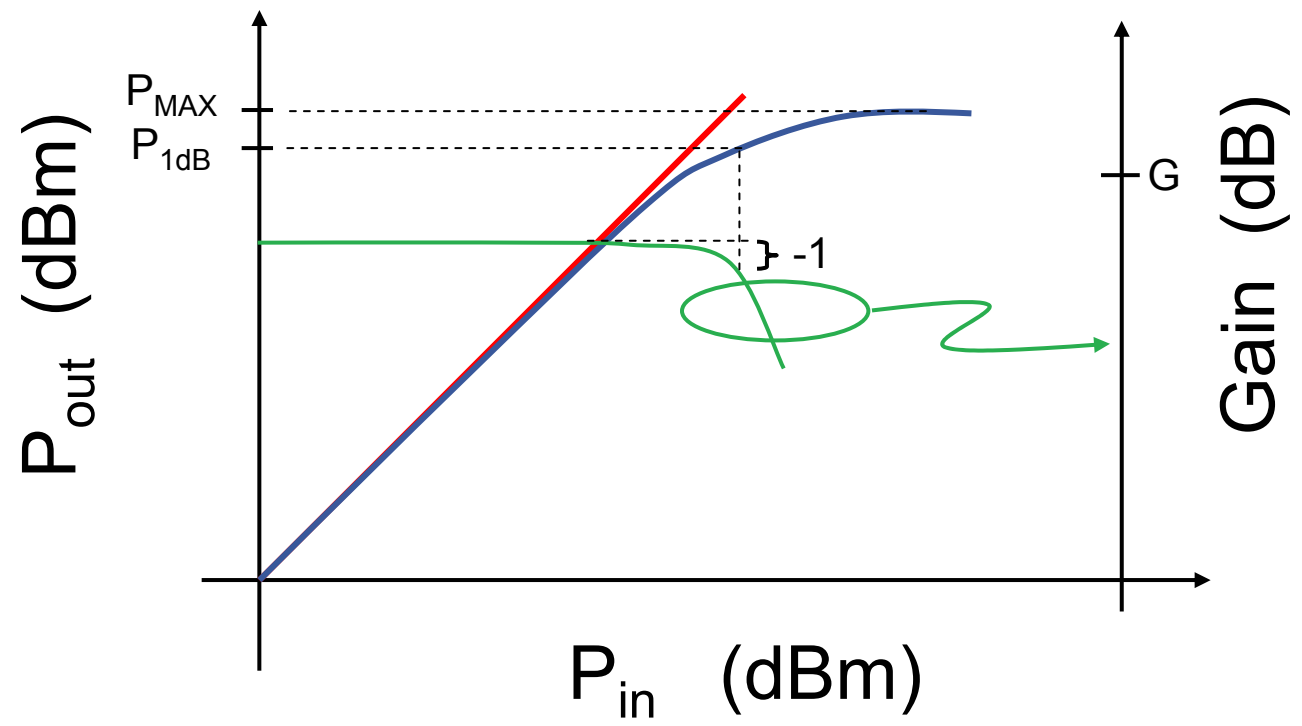



PA Introduction: Intrinsic PA Metrics

- ◆ **$P_{1\text{dB}}$** : Output power at which linear gain has compressed by 1dB (measure of linear power handling)
- ◆ **P_{MAX}** : Maximum output power (saturated power)
- ◆ **Gain**: Generally taken to mean transducer gain

$$\frac{\text{Power delivered to load}}{\text{Power available from source}}$$


- ◆ **PAE: Power-added Efficiency**

$$\frac{\text{Power to load} - \text{Power from source}}{\text{Power from supply}}$$



Linear and Non-linear PAs

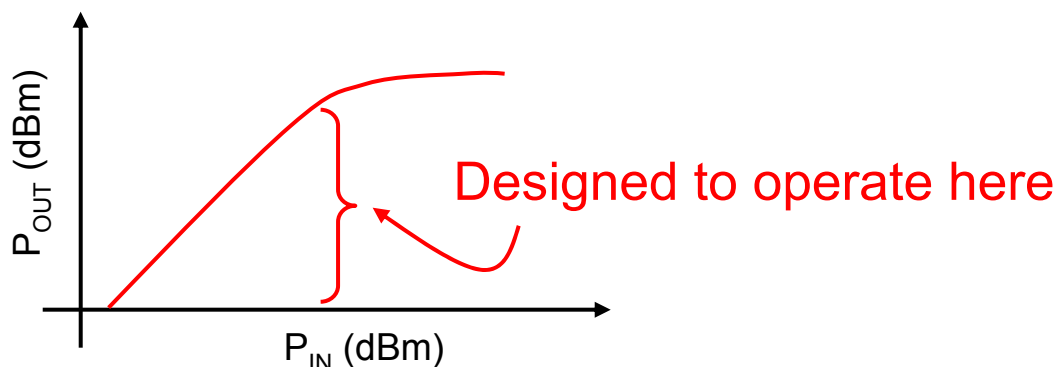- ◆ “Linear PA” generally refers to a PA which operates at constant gain, needs to preserve amplitude information




- ◆ Not necessarily class A (will discuss later ...) Peak efficiencies often only 40 to 45 %
- ◆ Useful for modulation schemes with amplitude modulation (QPSK, 8-PSK, QAM)



Linear and Non-linear PAs

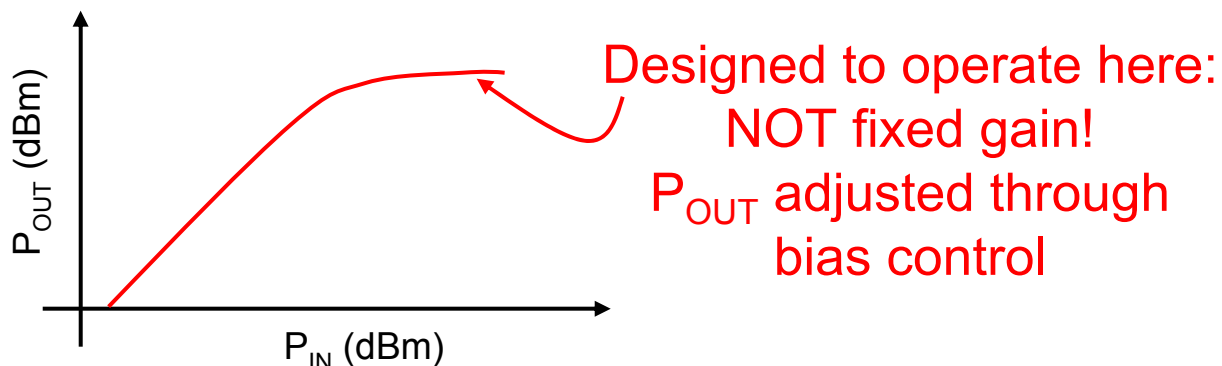
- ◆ “Non-linear PA” generally refers to a PA designed to operate with constant P_{IN} , output power varies by changing gain



- ◆ Operation in saturated mode leads to high peak efficiencies $> 50\%$; “backed-off” efficiencies drop quickly
- ◆ Useful for constant-envelope modulation schemes (GMSK)


PA Architectures

Typical 2-stage (6.012) design

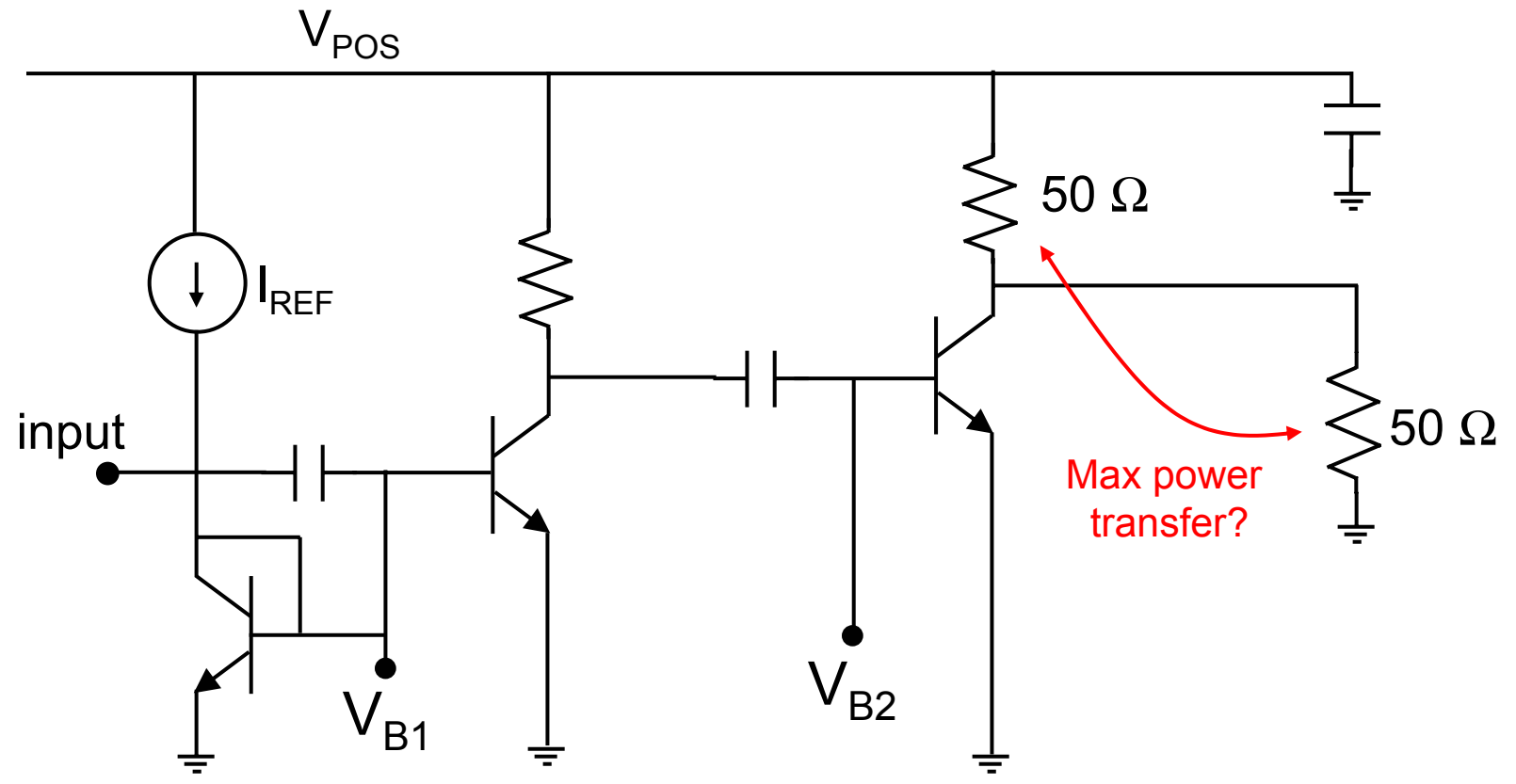


PA Architectures

Typical 2-stage RF PA design

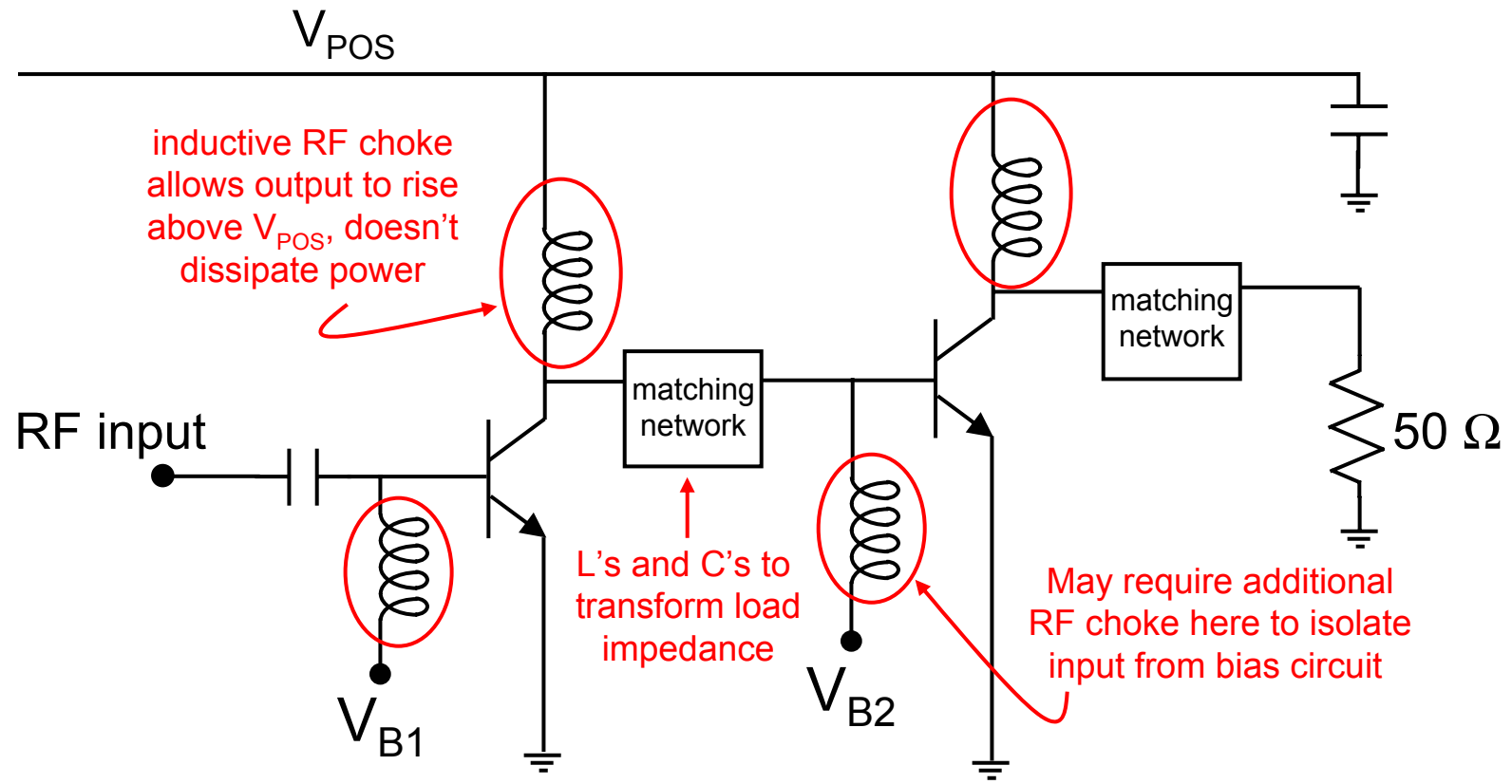

PA Architectures


Typical 2-stage RF PA design

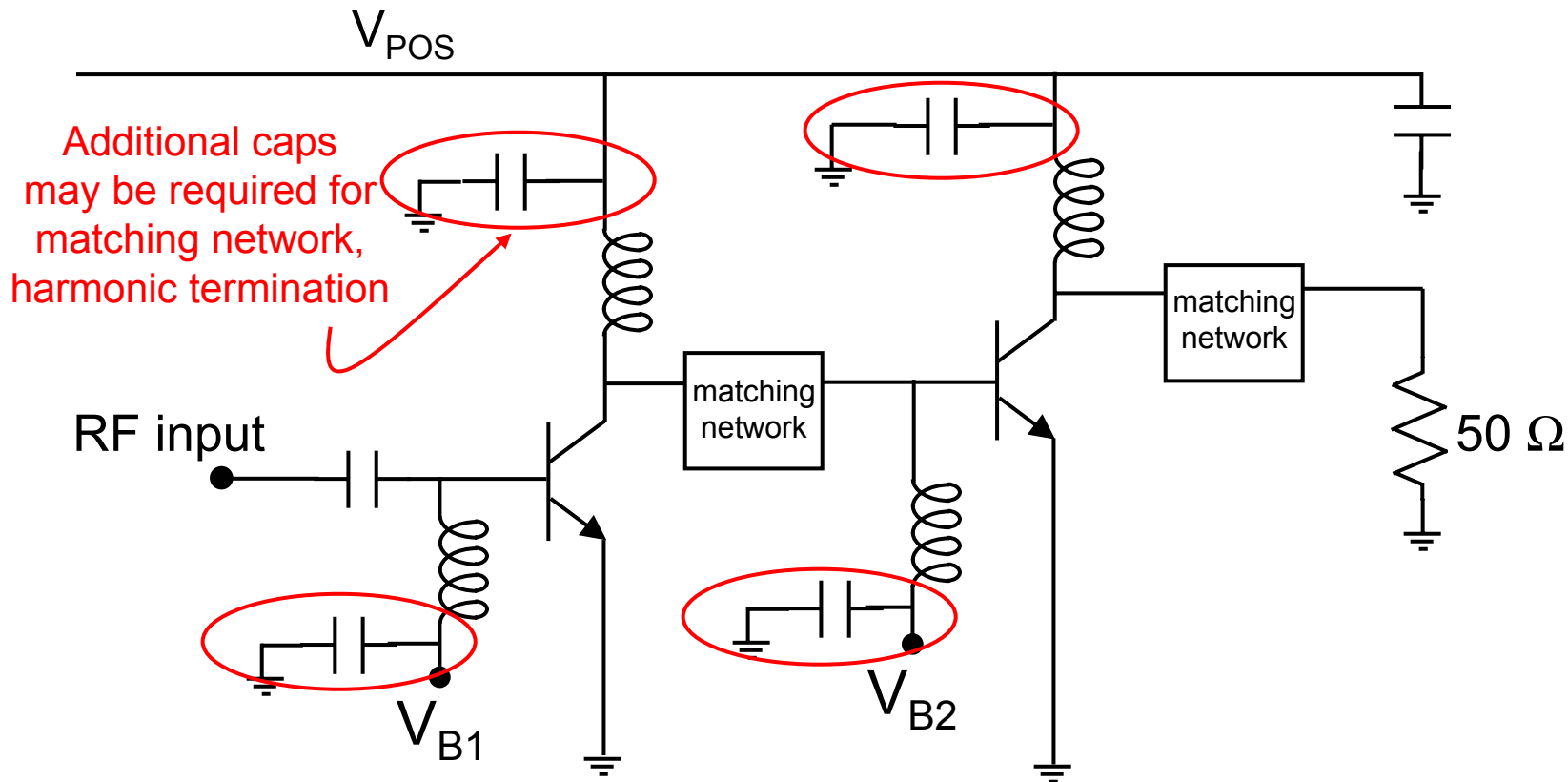



PA Architectures


Typical 2-stage RF PA design

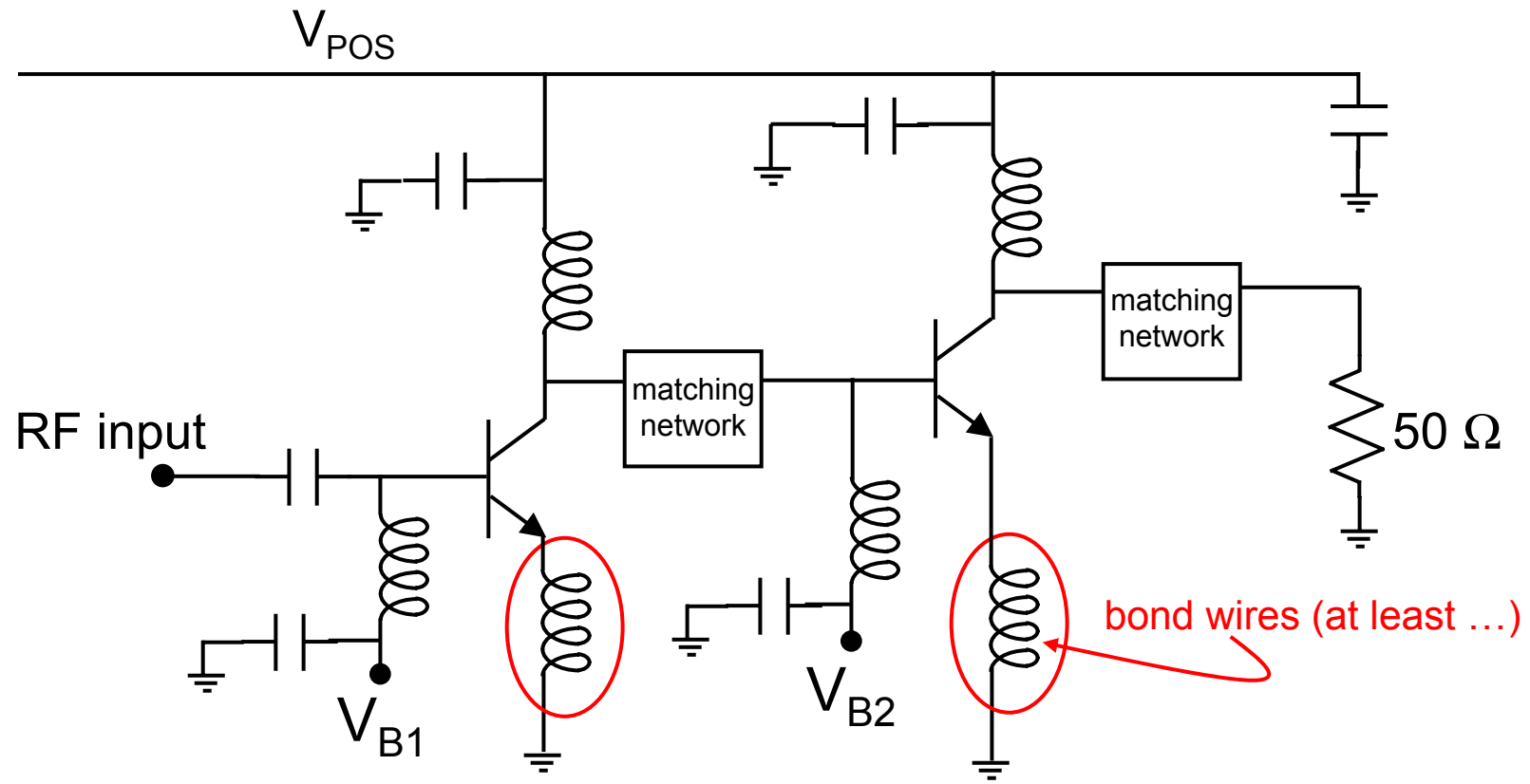



PA Architectures

Typical 2-stage RF PA design

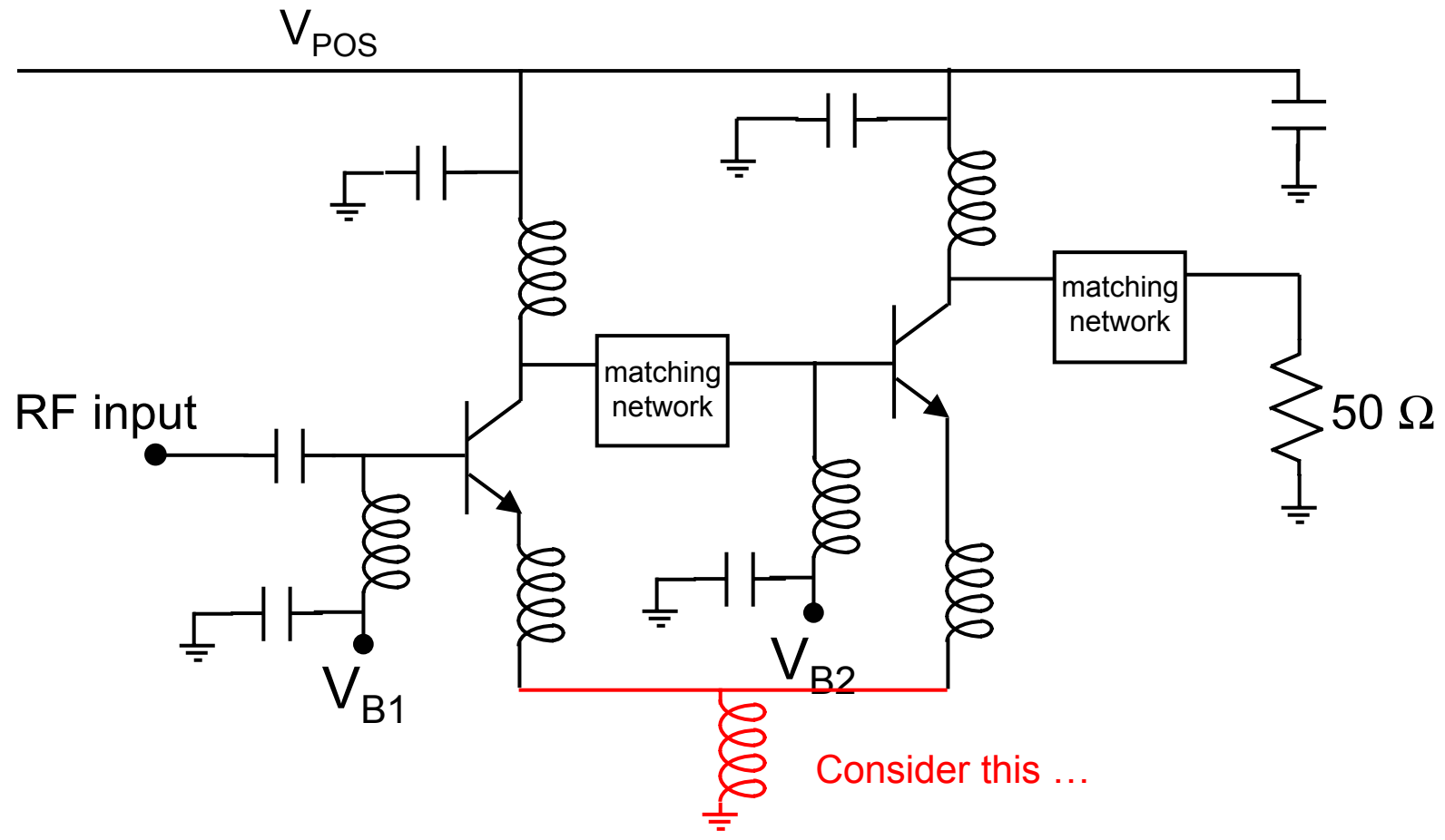




PA Architectures

- ◆ “Gain stage” is one transistor with passive elements
- ◆ “Active” components often limited to 2 or 3 transistors (gain stages) in signal path
- ◆ Transistor design very important!
 - Many parallel transistors – often look like mini-circuits themselves
- ◆ Passive components just as important as transistors!
 - Circuits must be tunable to account for uncertainties in determining values *a priori* (i.e. simulations stink – especially large-signal, RF simulations)
 - Q and parasitic elements of passives important



Single-Stage Linear PA

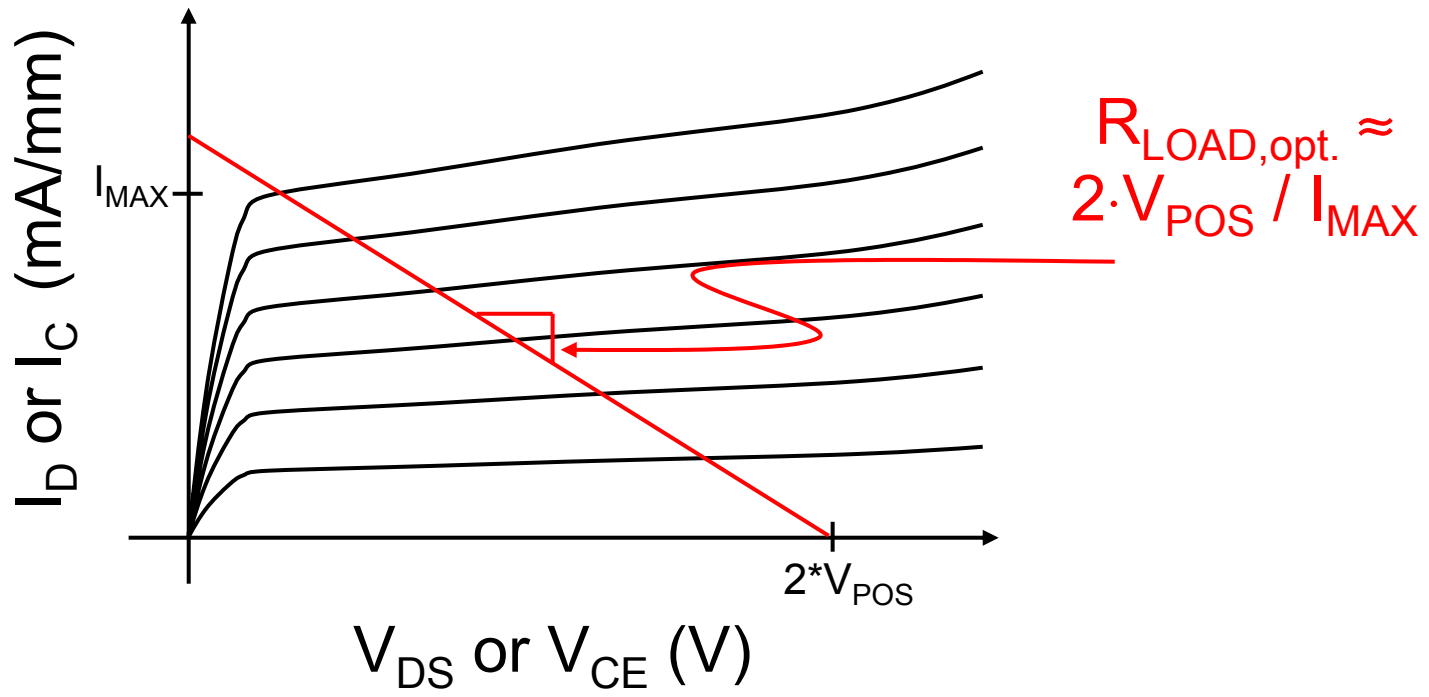- ◆ **Load-line theory:** the maximum power that a given transistor can deliver is determined by the power supply voltage and the maximum current of the transistor






Single-Stage Linear PA

- ◆ Transistor size chosen to deliver required output power

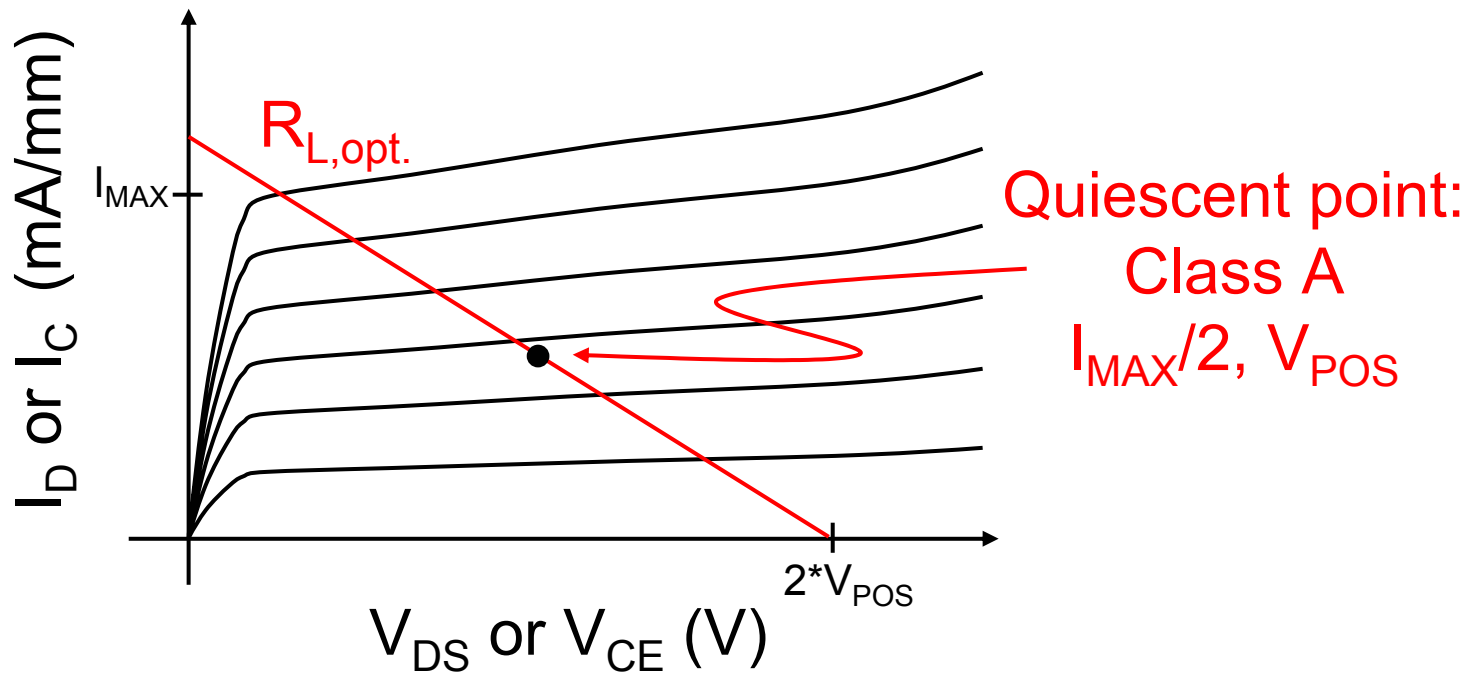
$$P_{OUT} \approx I_{MAX} \cdot V_{POS} / 4$$





Single-Stage, Linear PA

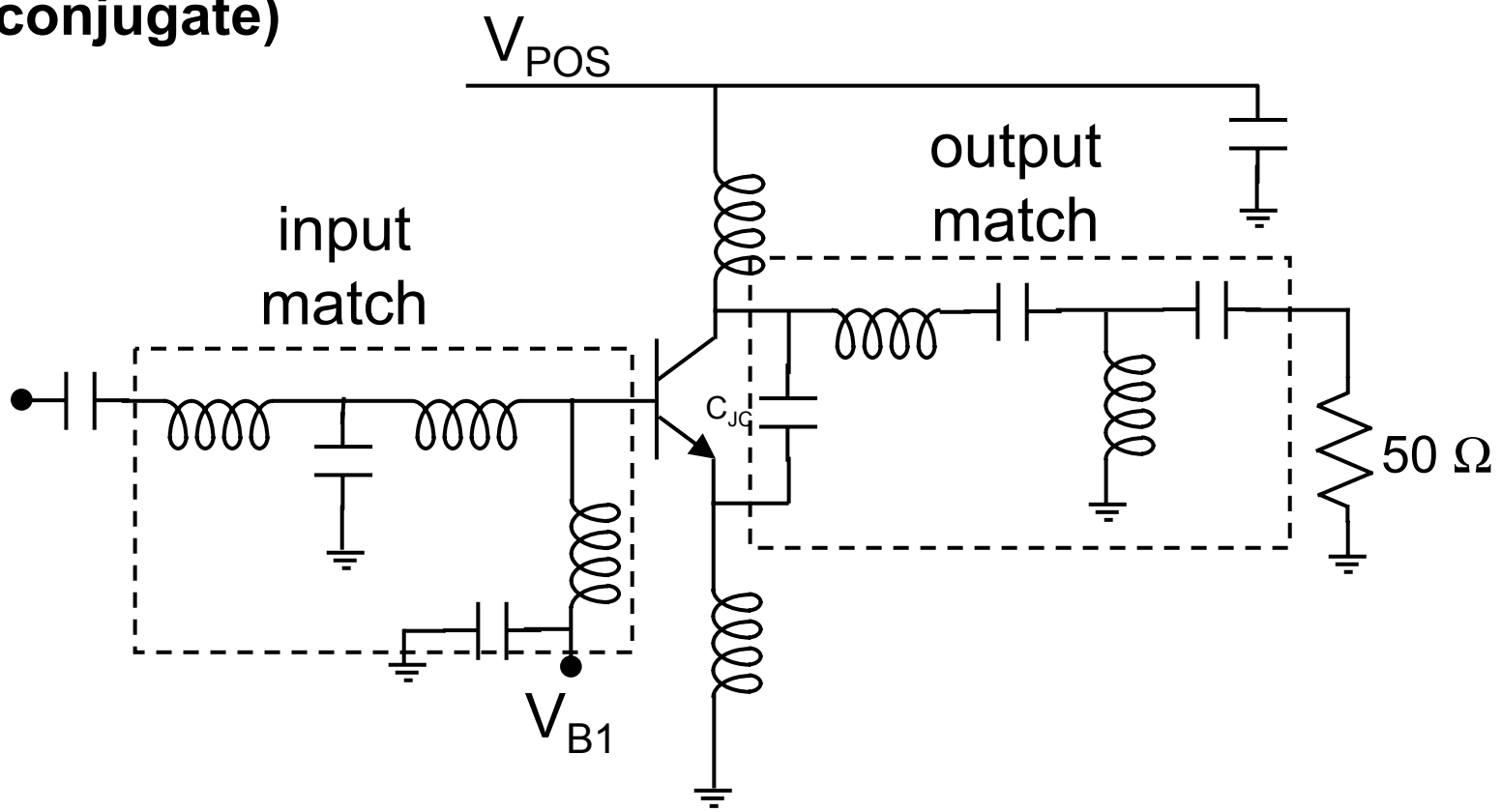- ◆ Design output match to transform 50Ω load to $R_{L,opt}$ at transistor output; then design input match for gain (complex conjugate)





Seems simple, so why is this so hard?

- ◆ **Determining I_{MAX} is not so easy**
 - For BJTs, one reference suggested that “the best way of estimating its value is to build an optimized class A amplifier and observe the dc supply current.”¹
 - Somewhat easier for depletion-mode GaAs FETs – I_{MAX} often corresponds to $V_{GS} = 0V$
 - Values don’t scale linearly with transistor size
- ◆ **Optimal load resistance only a theoretical number**
 - Transmission line effects, parasitic L’s and C’s significant at RF
 - Common practice is to vary the load of an actual transistor to determine the peak output power: the load-pull measurement
(Noticing a distinct pattern of “empirical” design emerging?)

¹ RF Power Amplifiers for Wireless Communications, Steve Cripps, Artech House, Boston, 1999.




Seems simple, so why is this so hard?

- ◆ **Now consider the problem for multiple stages ... double the trouble**
 - Typical single-stage gain only 10 – 15 dB
 - Inter-stage match now required to match input impedance of 2nd stage to desired output impedance of 1st stage.
- ◆ **Problems with matching circuits:**
 - Large matching ratios → high Q circuits for simple L matches
 - Multi-segment matches use valuable real estate, add cost
- ◆ **Transistor itself matters – a lot!**
 - Many parallel transistor
 - Ballasting, balancing and layout extremely important



High-efficiency PAs

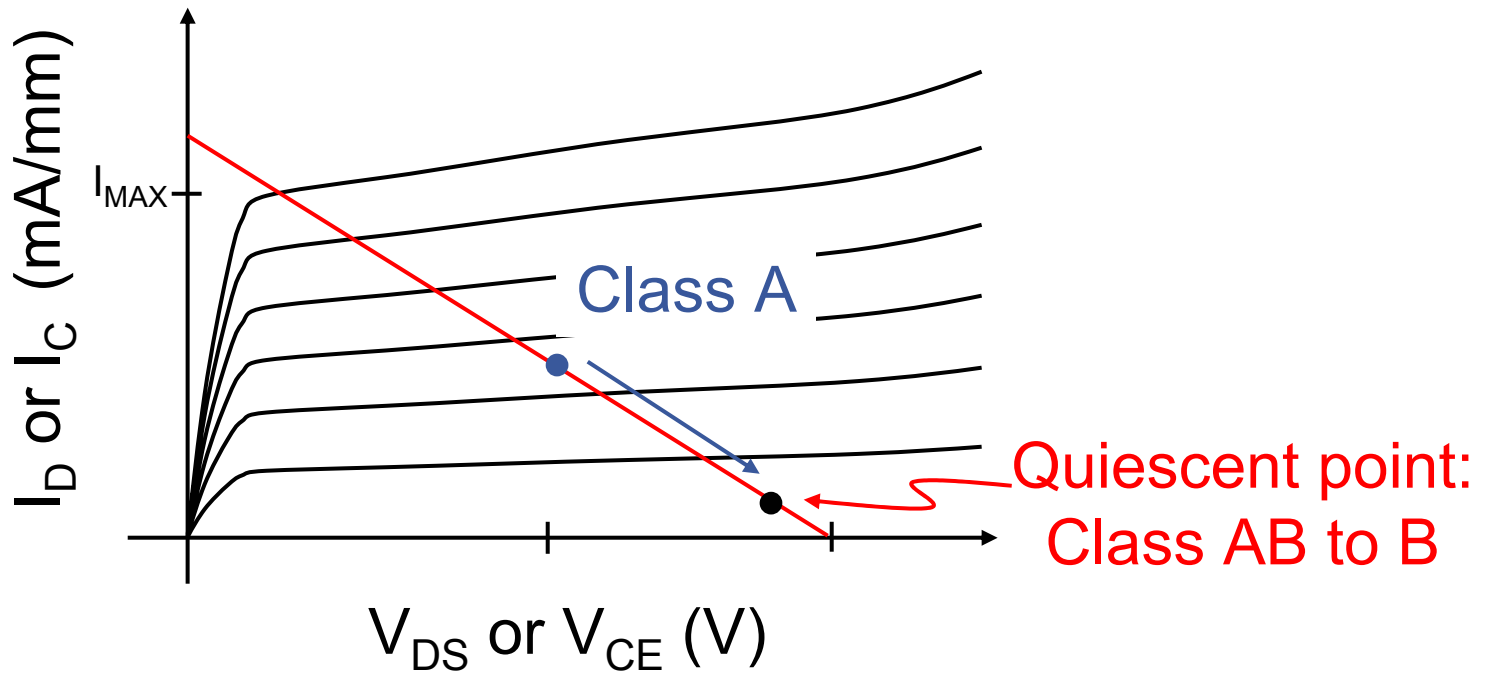- ◆ Input signal swing turns on transistor – conduction for only part of sinusoidal period






High-Efficiency PAs


Conduction Angle:

Class A:

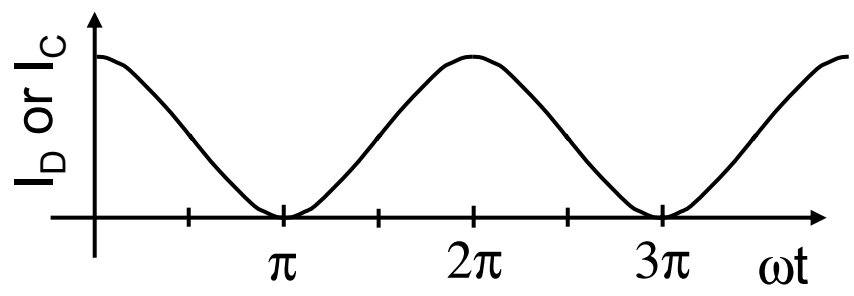


$$\alpha = 2\pi$$

Class AB:

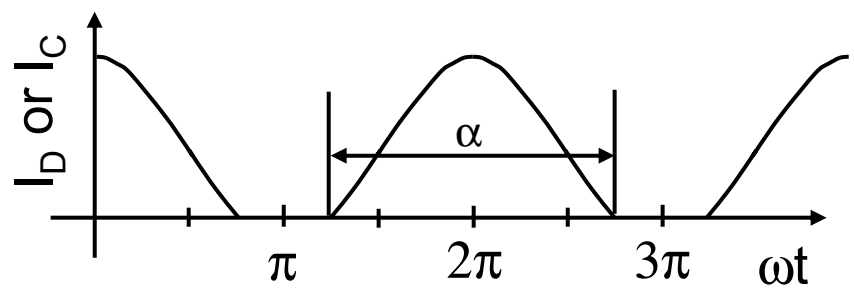

$$\pi < \alpha < 2\pi$$

Class B:

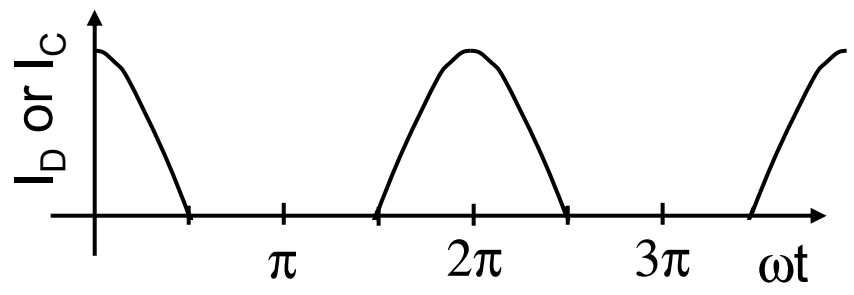


$$\alpha = \pi$$

Class C: $\alpha < \pi$

High-Efficiency PAs

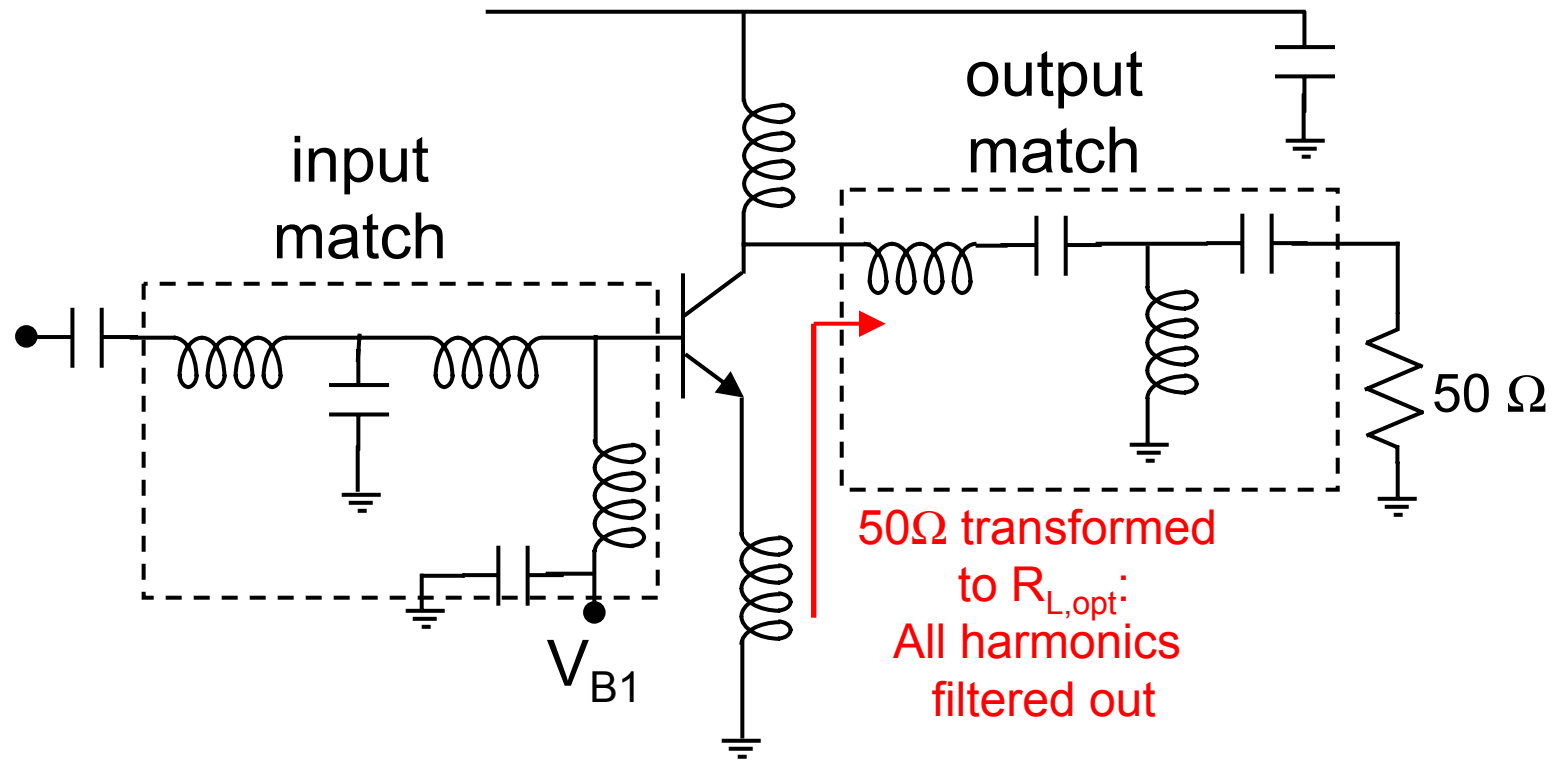
- ◆ Assume output match will filter out non-linearities caused by discontinuous conduction:





High-Efficiency PAs

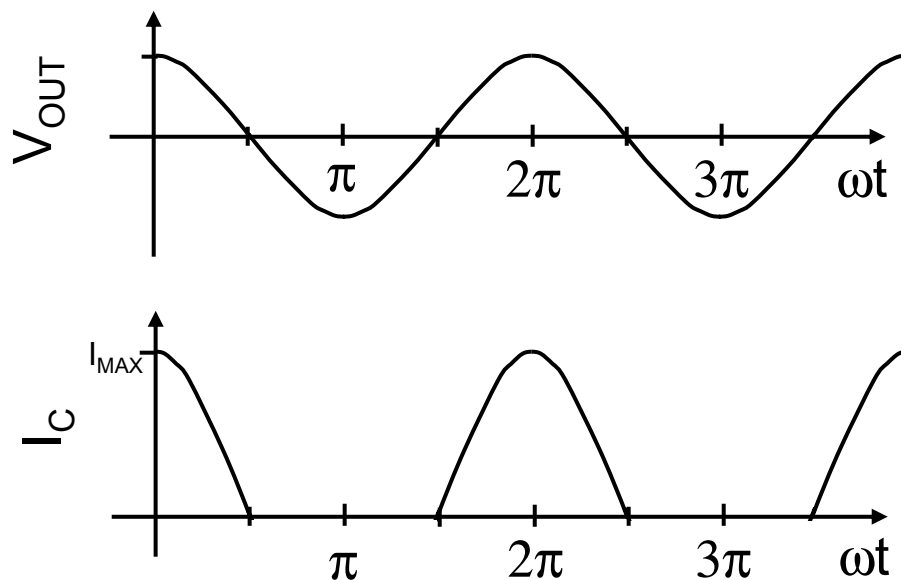- ◆ If all harmonics filtered out, then voltage output at load is a pure sinusoid, despite discontinuous conduction



- ◆ Energy stored in reactive elements delivers current to the load during transistor off-portion of cycle




High-Efficiency PAs

◆ Now consider peak efficiencies

Calculate fundamental component of current*

$$I_{dc} = (1/2\pi) \int_{-\alpha/2}^{\alpha/2} I_Q + I_{pk} \cos(\omega t) d\omega t$$
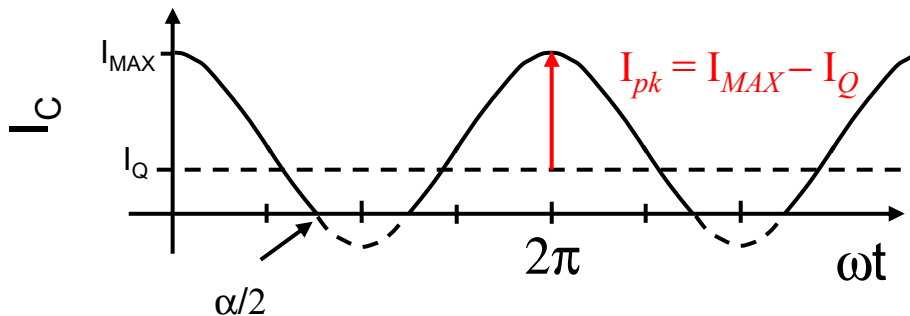
$$I_n = (1/\pi) \int_{-\alpha/2}^{\alpha/2} I_{pk} \cos(\omega t) \cos(n\omega t) d\omega t$$



* There are many texts which cover reduced-conduction angle calculations. See for example *Principles Of Power Electronics*, Kassakian, Schelcht and Verghese, Ch. 3.



High-Efficiency PAs

From phasor plot: $\cos(\alpha/2) = -I_Q / I_{pk} = -I_Q / (I_{MAX} - I_Q)$

Put it all together and do the math, you get:

$$I_{dc} = \frac{I_{MAX}}{2\pi} \frac{2\sin(\alpha/2) - \alpha\cos(\alpha/2)}{1 - \cos(\alpha/2)}$$

$$I_{1,0-p} = \frac{I_{MAX}}{2\pi} \frac{\alpha - \sin\alpha}{1 - \cos(\alpha/2)}$$

Assume V_{OUT} the same for all classes:

$$V_{1,0-p} = V_{POS}$$



High-Efficiency PAs

◆ Summary of PA “ideal” peak efficiencies

Class A:
$$\frac{P_1}{P_{dc}} = \frac{(I_{MAX}/2) / \sqrt{2} \cdot V_{POS} / \sqrt{2}}{(I_{MAX}/2) \cdot V_{POS}} = 50 \%$$

Class B:
$$\frac{P_1}{P_{dc}} = \frac{(I_{MAX}/2) / \sqrt{2} \cdot V_{POS} / \sqrt{2}}{(I_{MAX}/\pi) \cdot V_{POS}} = 78 \%$$


Class C: Ideally can go to 100%, but P_1 drops steadily beyond $\alpha=\pi$, goes to 0 at 100%!



High-Efficiency PAs

◆ What happened to our load line?

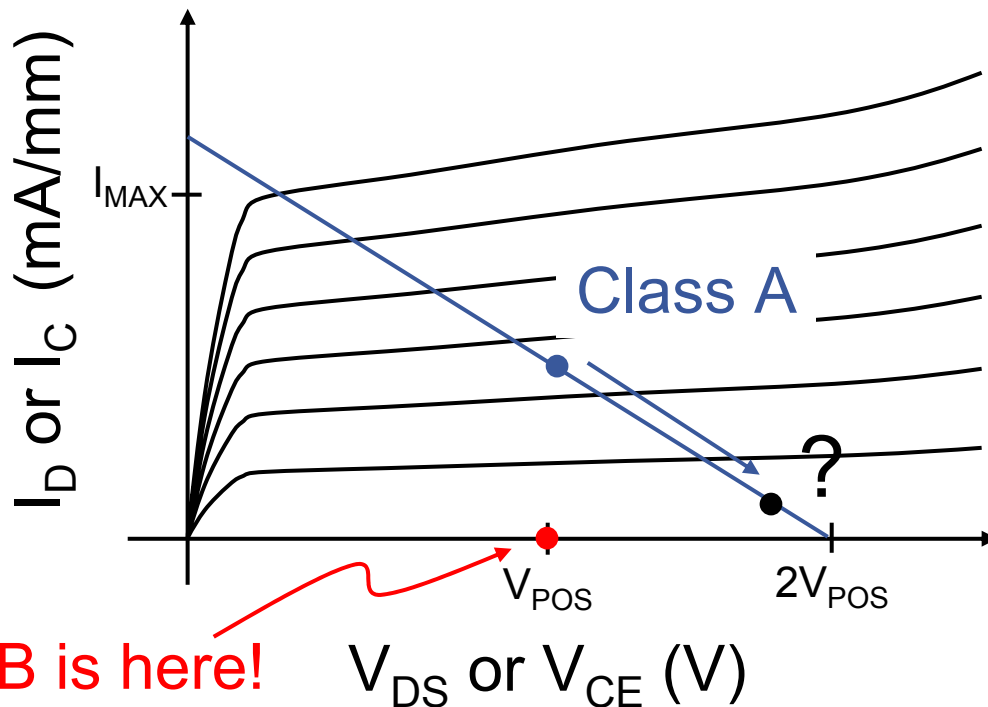- For class B fundamental $R_{L,opt} = V_{POS}/(I_{MAX}/2)$ – Didn't change




Class B is here!



High-Efficiency PAs

◆ What happened to our load line?

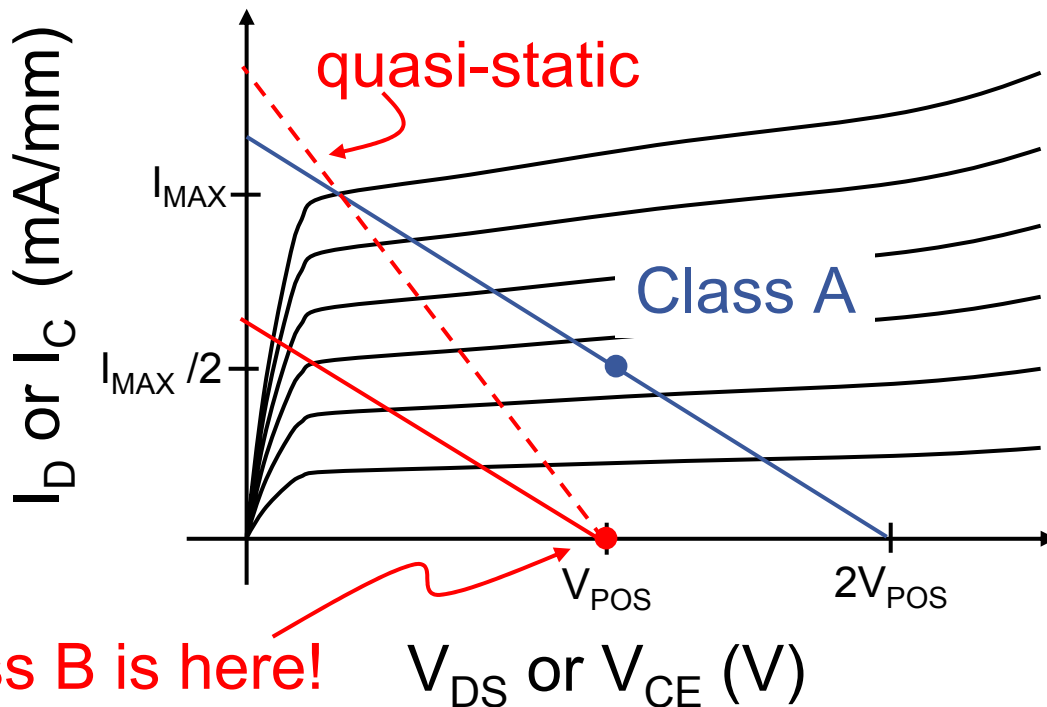- For class B fundamental $R_{L,opt} = V_{POS}/(I_{MAX}/2)$ – Didn't change



In quasi-static picture, resistance presented to transistor output cut in half. But average resistance is the same for class A




High-Efficiency PAs

◆ Now consider “linearity”

- Clearly the current waveforms are far from linear

BUT ...

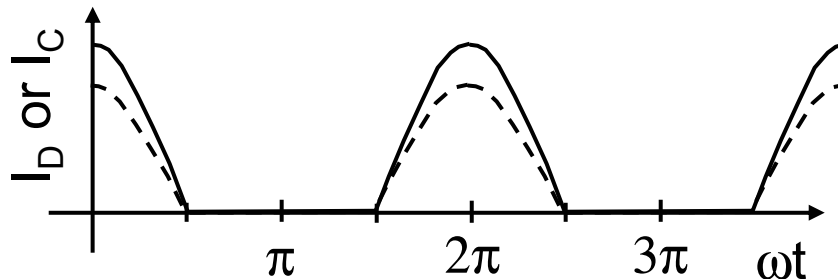- Overall P_{OUT} vs. P_{IN} transfer function can still be quite linear, especially for true Class B where output current waveform is symmetrical with respect to input waveform



Because conduction angle is constant,
 P_{OUT} changes proportional to P_{IN}



Real-World Design Example

◆ IDEAL: Design each stage independently

- Determine required gain – number of stages
- Determine P_{OUT} for each stage
- Determine $R_{L,opt}$ for each stage
- Determine input impedance for each stage
- Design matching networks for inter-stage, load and input

◆ REALITY:

- I_{MAX} doesn't scale nicely with transistor size. Without good I_{MAX} numbers, can't determine $R_{L,opt}$. Need to do load-pull.
- Even load pull measurements have limited accuracy for very large transistors
- Designs are very empirically driven!



Real-World Design Example

GSM 900 MHz, GaAs HBT PA Design

◆ $P_{OUT} = 33 \text{ dBm (linear)} = 2 \text{ W}$

$$V_{CC} = 3.5\text{V}$$

$$R_{LOAD} = V_{CC}^2 / 2 * P_{OUT} = 3 \Omega$$

$$I_{MAX} = 2 * V_{CC} / R_{LOAD} = 2.33 \text{ A}$$

(Note: expect saturated power to be ~ 35 dBm)

◆ Input power: constant-envelope +5 dBm

◆ Gain = $P_{OUT} - P_{IN} = 27 \text{ dB}$.

◆ Expect roughly 10 dB per stage



3 STAGE DESIGN



Real-World Design Example

- ◆ **Stage 1: Gain = 10 dB → P_{OUT} = 15 dBm**
 - $R_{L1} = V_{CC}^2 / 2 * P_{OUT} = 194 \Omega$
 - $I_{MAX} = 2 * V_{CC} / R_{LOAD} = 36 \text{ mA}$
 - Chose class A: $I_{DC} = I_{MAX} / 2 = 18 \text{ mA}$
(18 mA insignificant compared to 2.33 A)
- ◆ **Stage 2: Gain = 10 dB → P_{OUT} = 25 dBm**
 - $R_{L2} = 19.4 \Omega$
 - $I_{MAX} = 360 \text{ mA}$
 - Still probably class A (maybe AB): $I_{DC} = I_{MAX} / 2 = 180 \text{ mA}$
- ◆ **Stage 3: Gain = 7 dB → P_{OUT} = 33 dBm**
 - $R_{L2} = 3 \Omega, I_{MAX} = 2.33 \text{ A}$
 - Class B: $I_{DC} = I_{MAX} / \pi = 742 \text{ mA}$



Real-World Design Example

A note on “Gain”

◆ Taking a very simplistic view of common emitter stages:

- $g_{m1} = I_C / V_{Th} = 18 \text{ mA} / 0.025 \text{ V} = 0.696 \text{ S}$
- $g_{m1} R_{L1} = 0.696 \cdot 194 = 135 \rightarrow \text{NOT } 10 \text{ dB!}$

BUT ...

- $r_{e1} = 1/g_{m1} = 1.44 \text{ } \Omega$
- $r_{e2} = 1/g_{m2} = 0.144 \text{ } \Omega$
- $r_{e3} = 1/g_{m3} = 0.035 \text{ } \Omega$

1. Remember it's power gain, not voltage gain. Can lose voltage at input match.
2. It's pretty tough not to get significant degeneration!



Real-World Design Example

◆ Efficiency calculations:


- $I_{DC1} = 18 \text{ mA}$, $I_{DC2} = 180 \text{ mA}$, $I_{DC3} = 742 \text{ mA}$
- Total DC Current: 940 mA

$$\frac{P_1}{P_{dc}} = \frac{(I_{MAX}/2) / \sqrt{2} \cdot V_{POS} / \sqrt{2}}{I_{DC} \cdot V_{POS}} = 62 \%$$

- Realistically may get as high as 55%

Real-World Design Example: Load-Pull

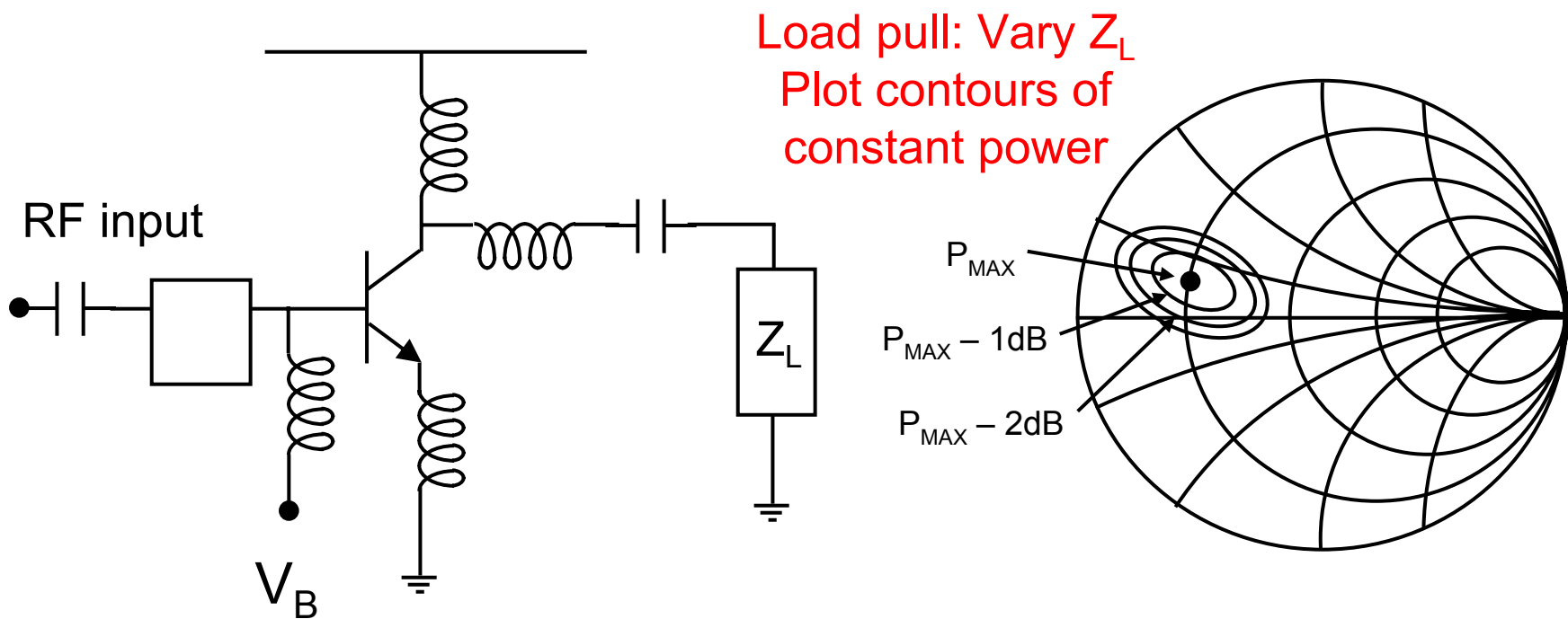- ◆ After initial “guesses” at transistor sizes, load-pull to determine actual target load for matching circuits






Real-World Design Example: Load-pull

Notes on load-pulling:


- ◆ Most accurate on probe station, but insertion loss of probes prevents it from being useful for large transistors (“Insertion loss” is RF code word for resistance)
- ◆ Bonded devices on evaluation board must be carefully de-embedded
- ◆ Even using electronic tuners, accuracy is poor for very large transistor (i.e. for loads in the 2 – 5 Ω range)

Real-World Design Example: The Circuit

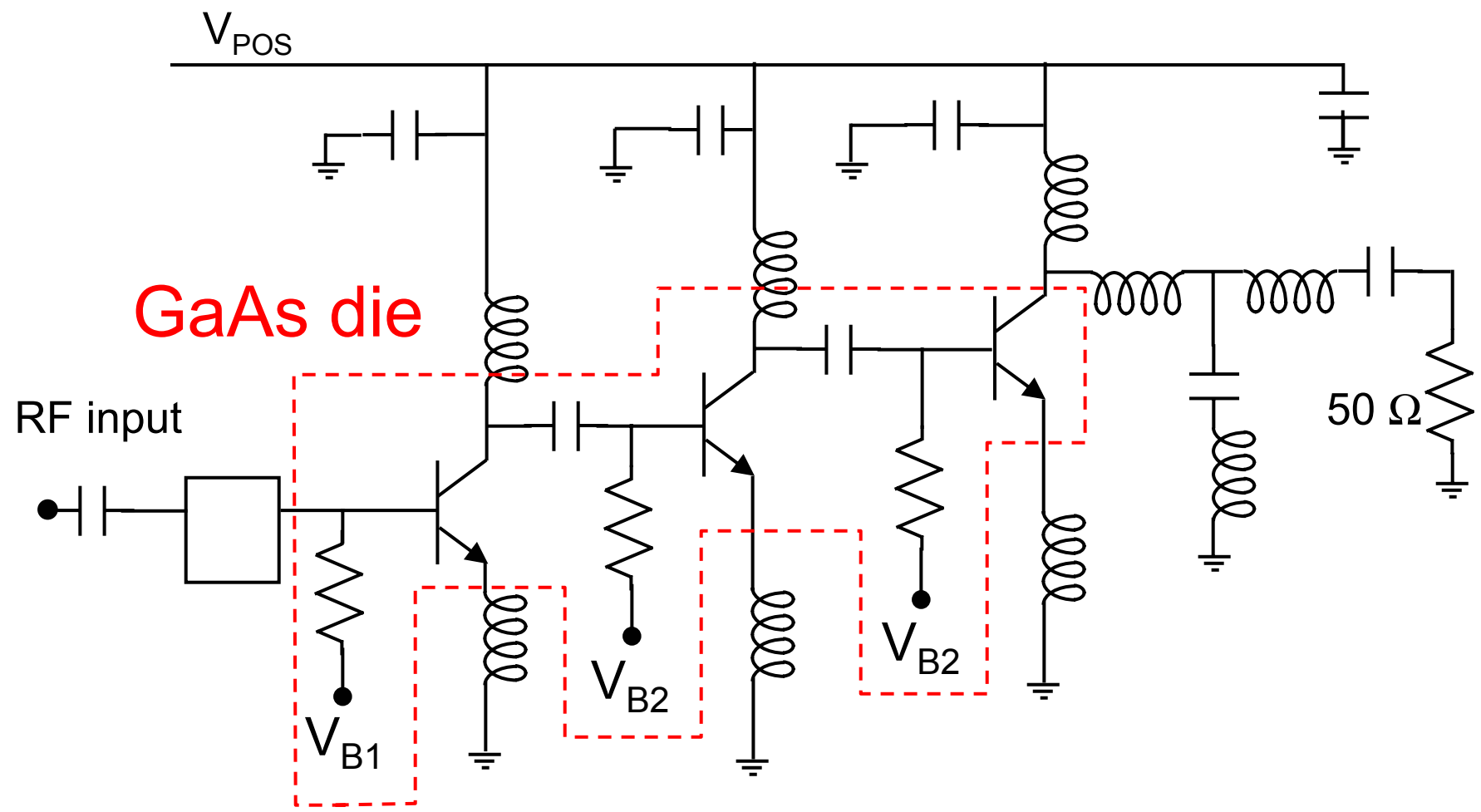





Real-World Design Example: The Circuit

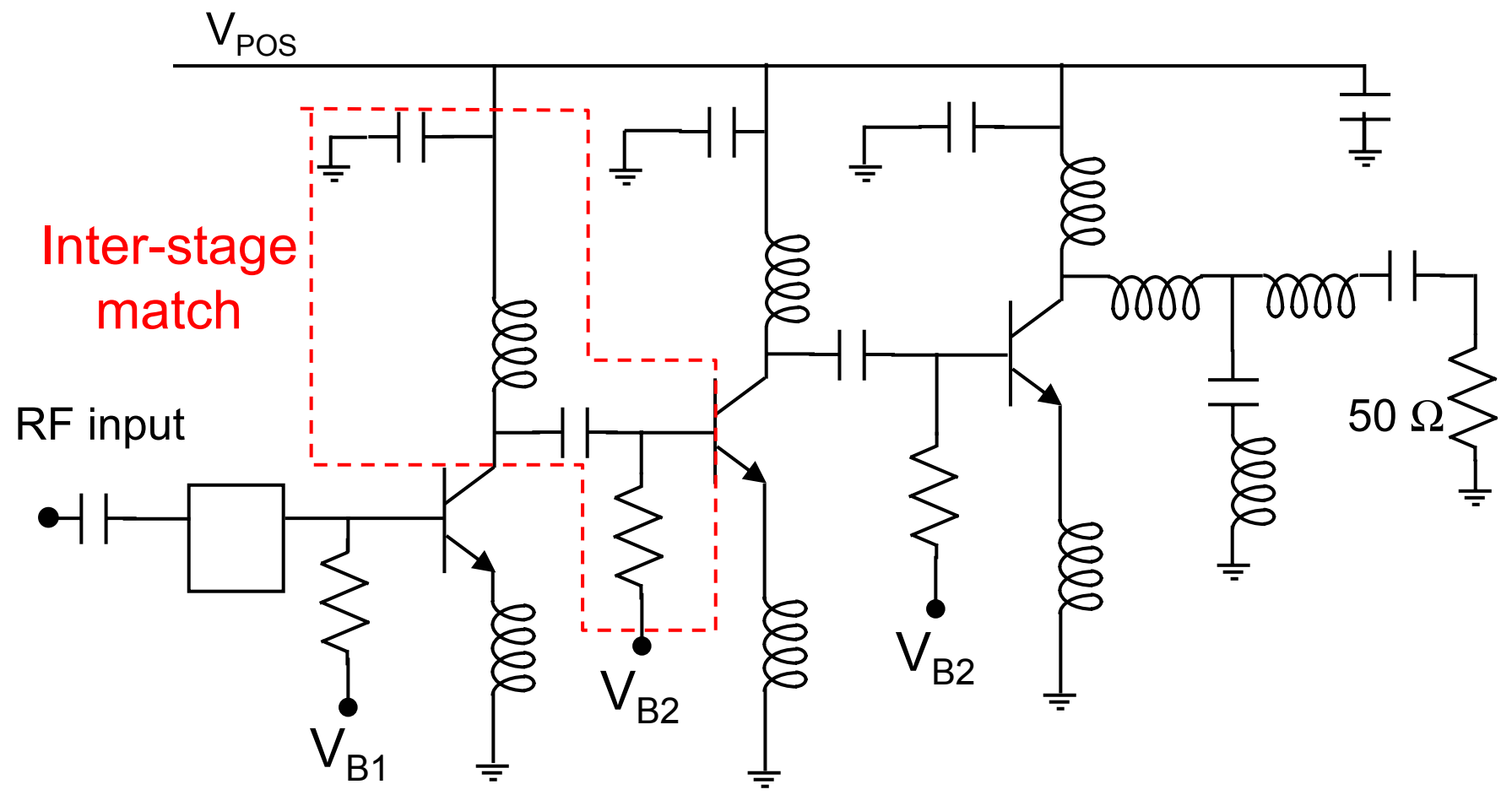

Real-World Design Example

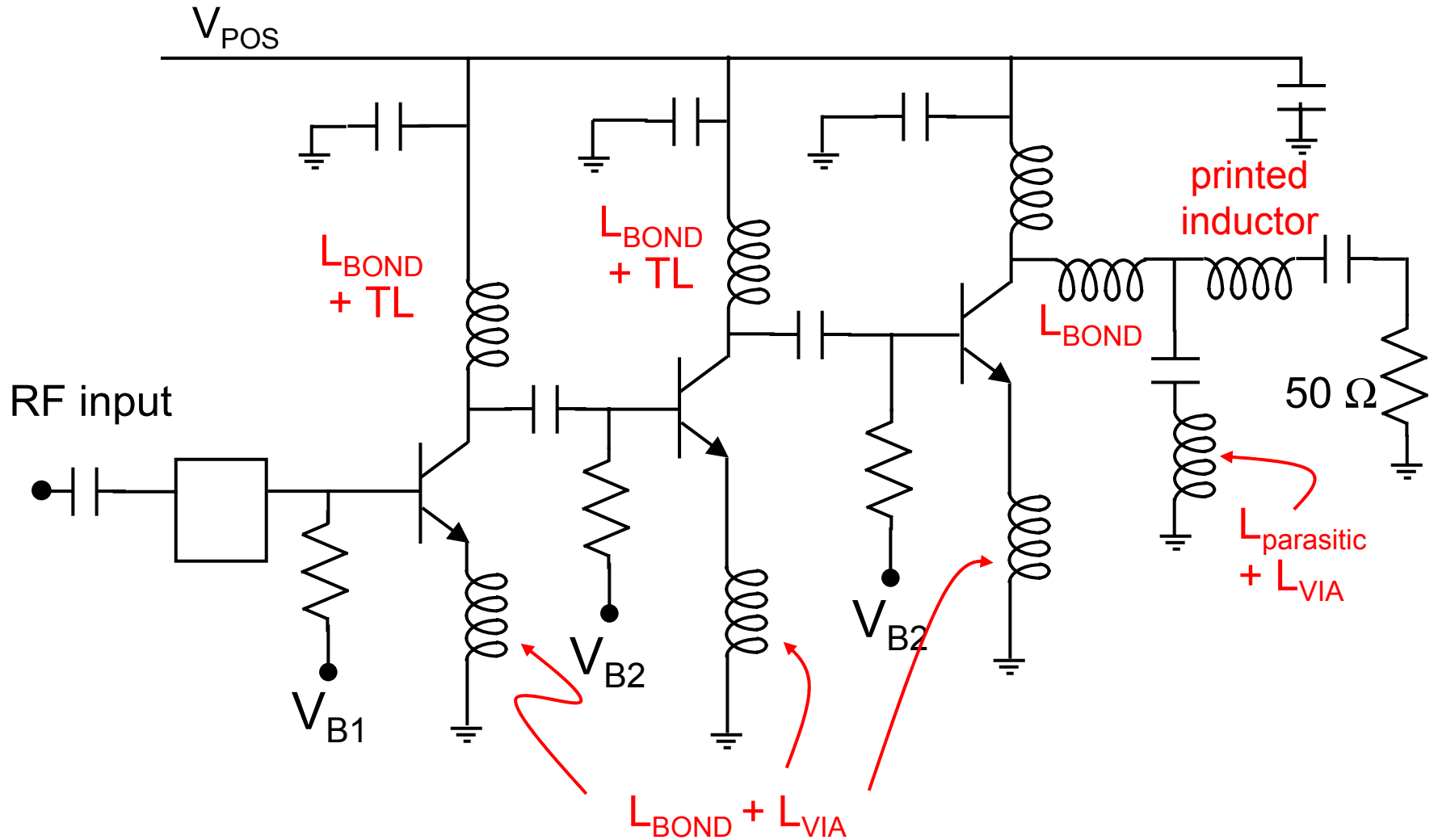

Real-World Design Example

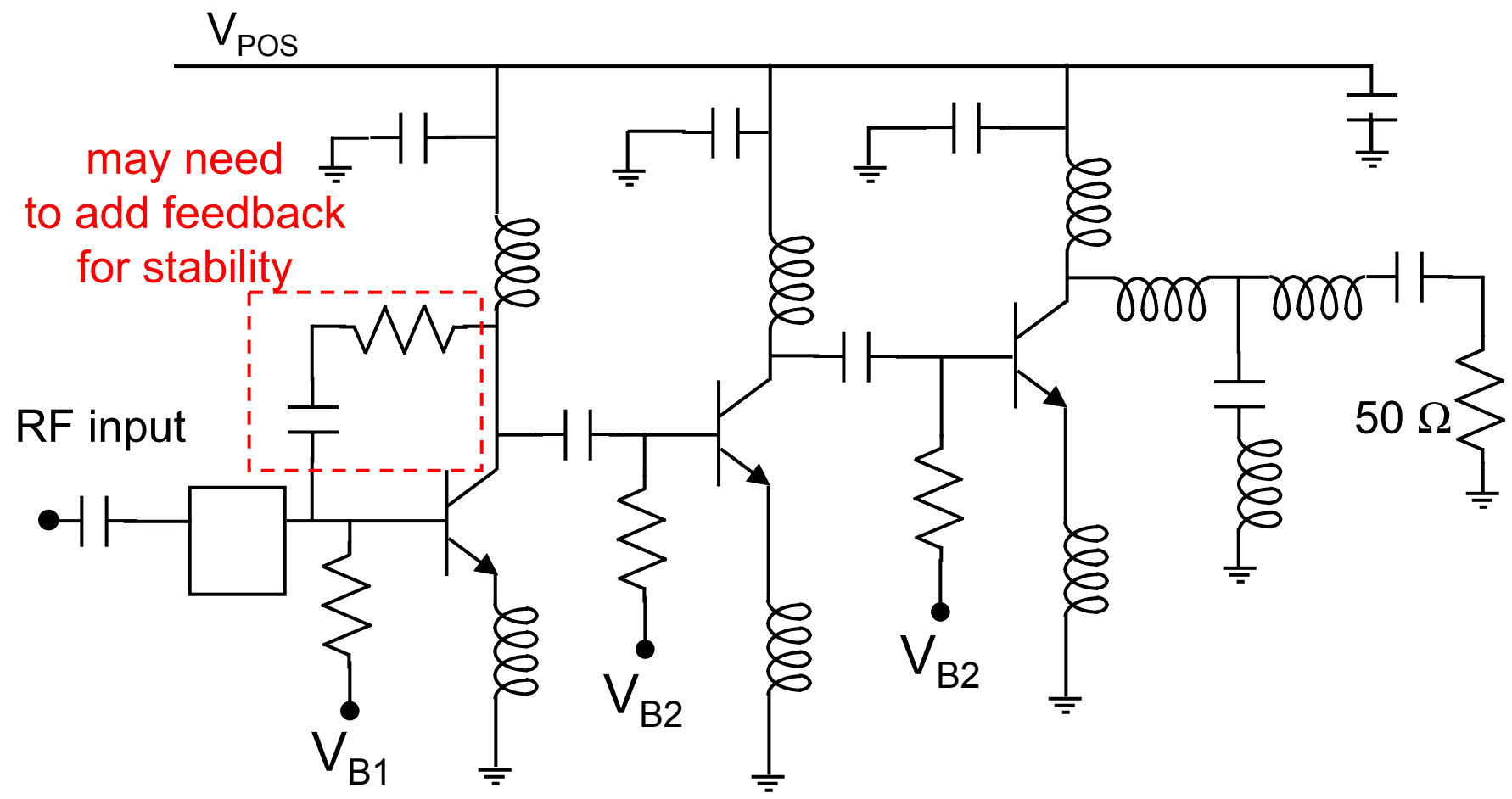


Real-World Design Example: Tuning

◆ Example of inter-stage match, 1st to 2nd stage

$$R_{L1} = 194 \Omega (?)$$

$$Z_{IN2} = 30 - j10 (?)$$

Both are really just guesses

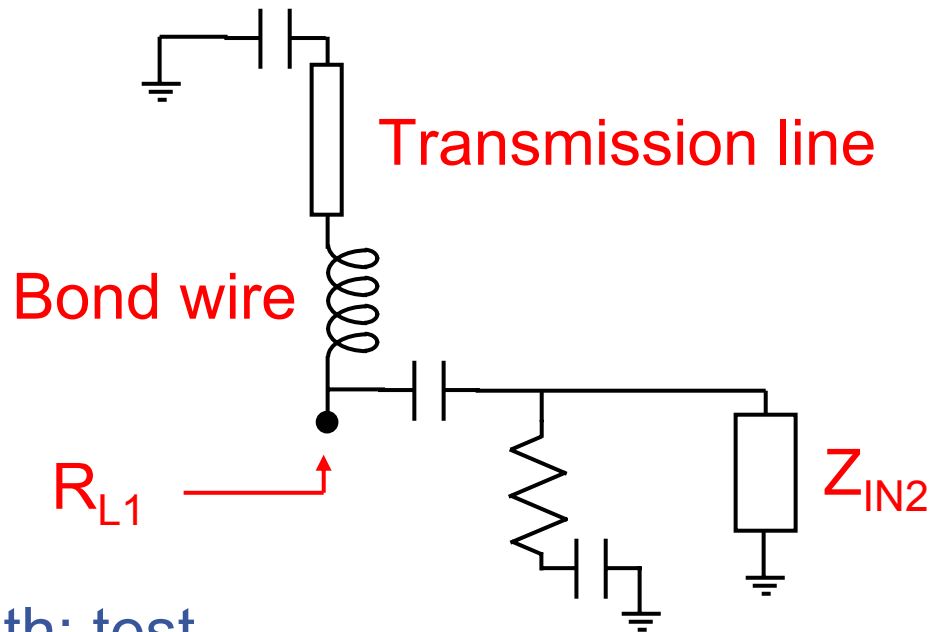


* Go to WinSmith: test

Real-World Design Example: Tuning

◆ Example of inter-stage match, 2nd to 3rd stage

$$R_{L2} = 19.4 \Omega$$

$$Z_{IN3} = 2 - j2$$

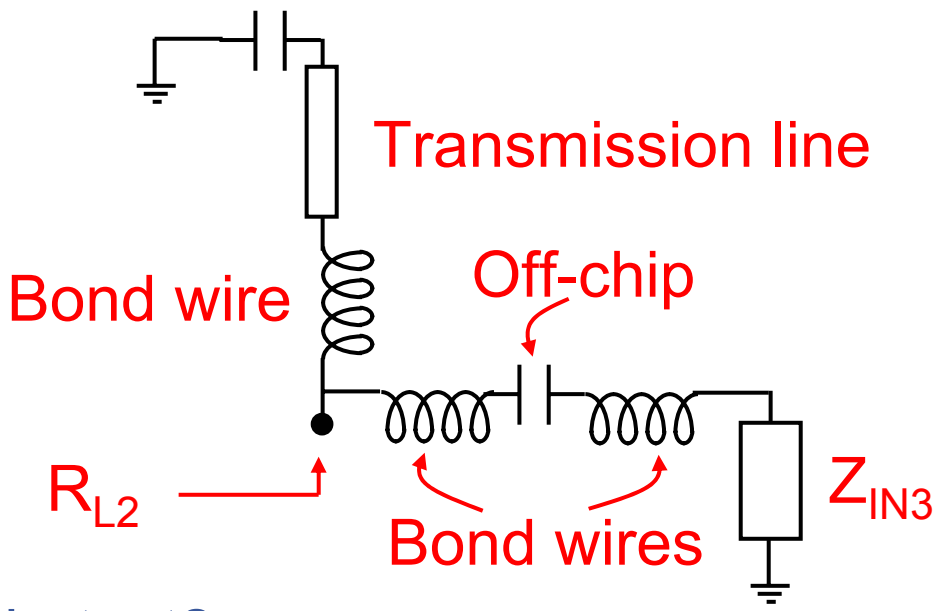


* Go to Winsmith: test2

System Specifications

◆ Ruggedness

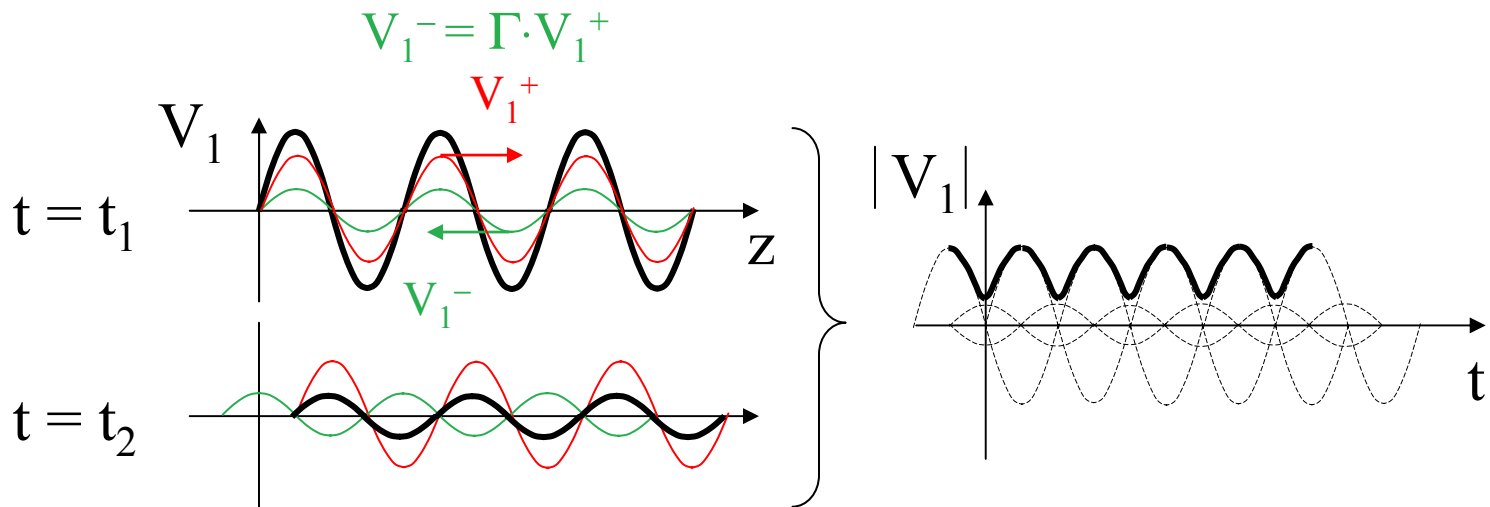- 50 Ω load is for antenna in free space. Place antenna on a metal plate and can easily get VSWR of 4:1
- Typical PA specs are: don't oscillate at up to 4:1, survive up to 10:1 (!)






System Specifications

◆ Linearity

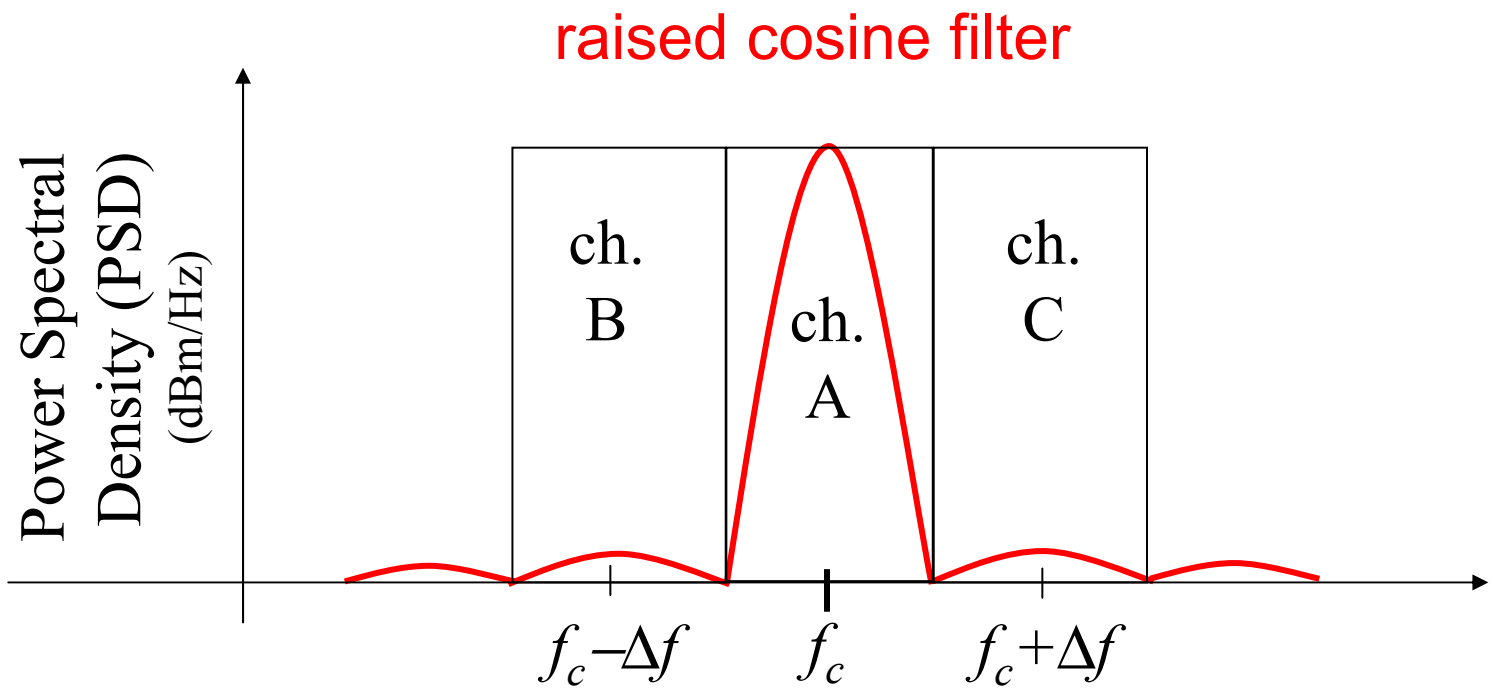- For linear PAs, Adjacent Channel Power Ratio (ACPR) is very important






System Specifications

◆ Linearity

 - For linear PAs, Adjacent Channel Power Ratio (ACPR) is very important






System Specifications

◆ Linearity

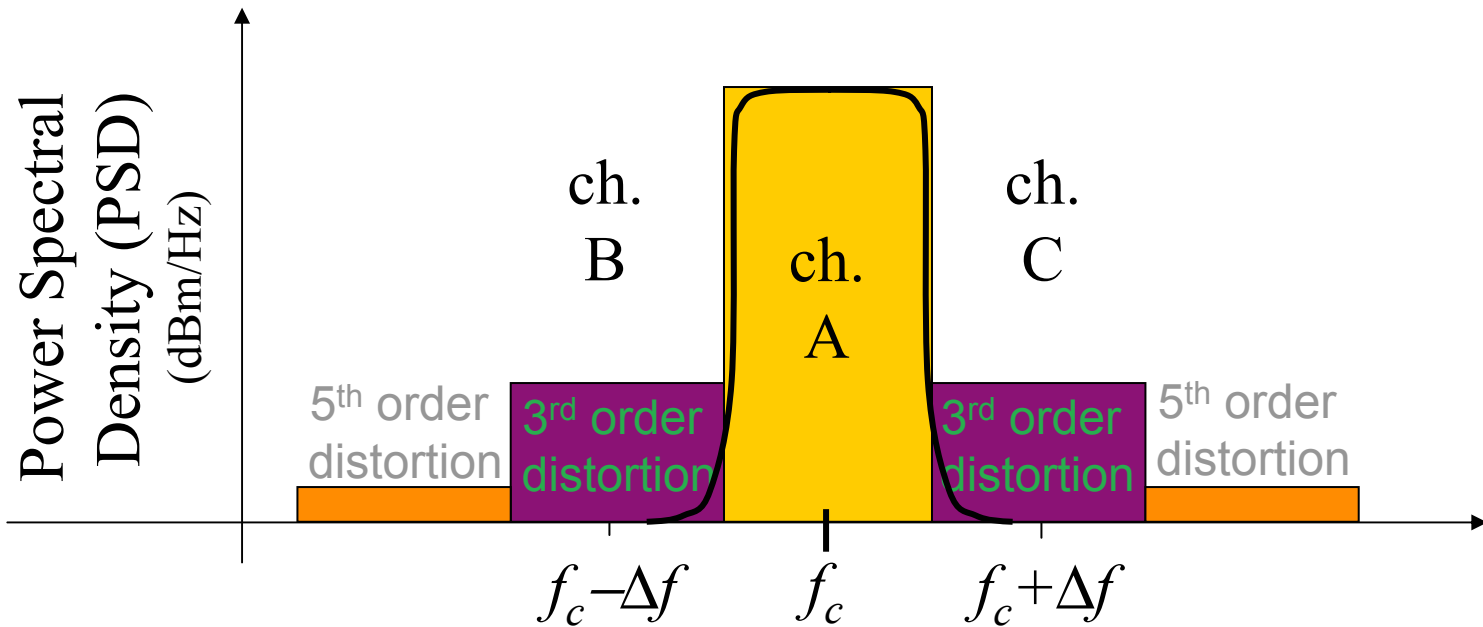- For linear PAs, Adjacent Channel Power Ratio (ACPR) is very important






System Specifications

◆ Linearity

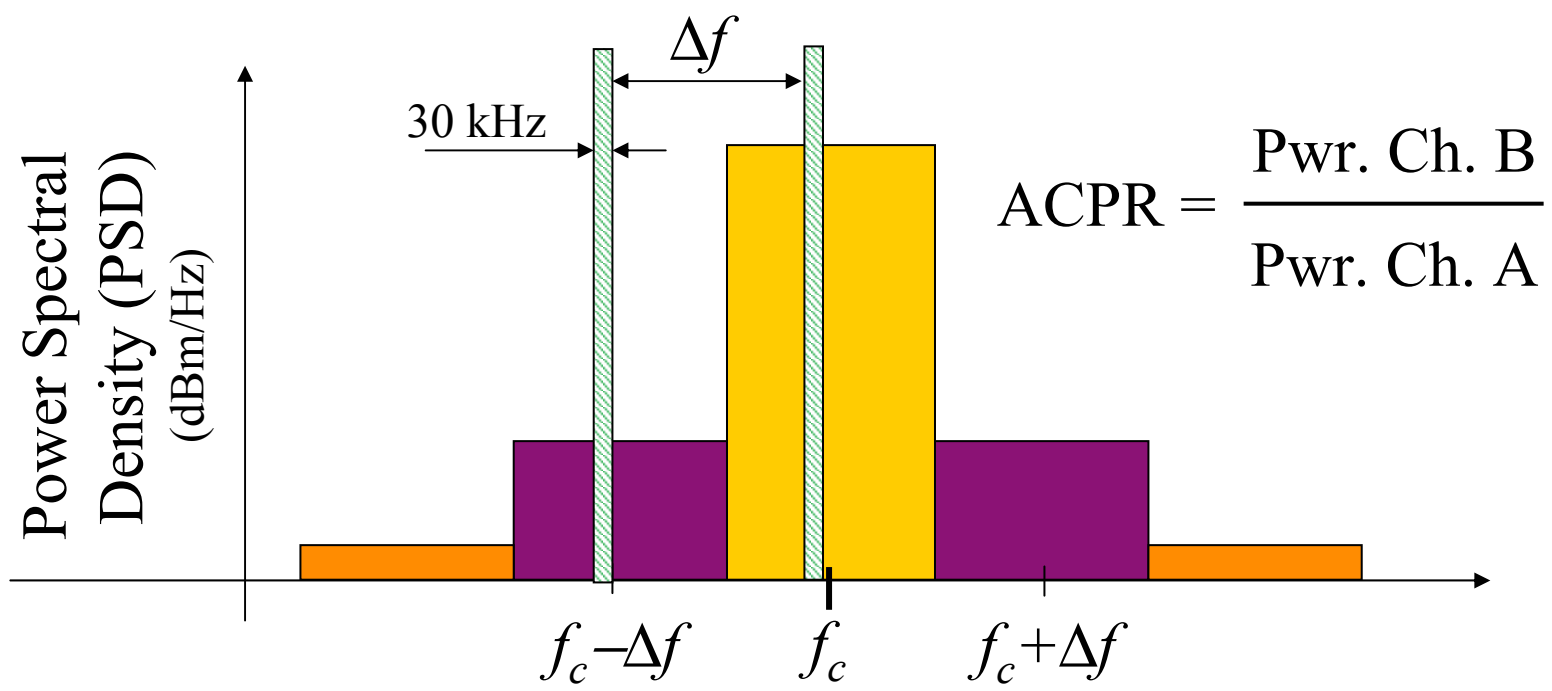- For linear PAs, Adjacent Channel Power Ratio (ACPR) is very important






System Specifications

◆ Linearity

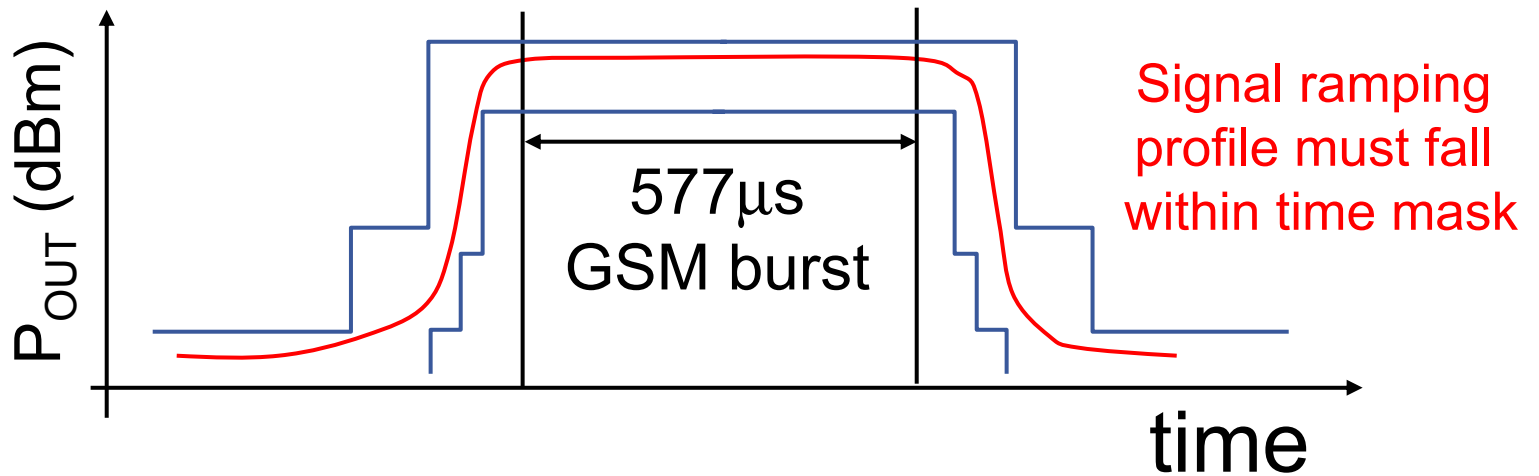- For non-linear PA in TDMA systems, harmonic spurs and switching transients are most common measure of linearity






System Specifications

◆ Noise in receive band:

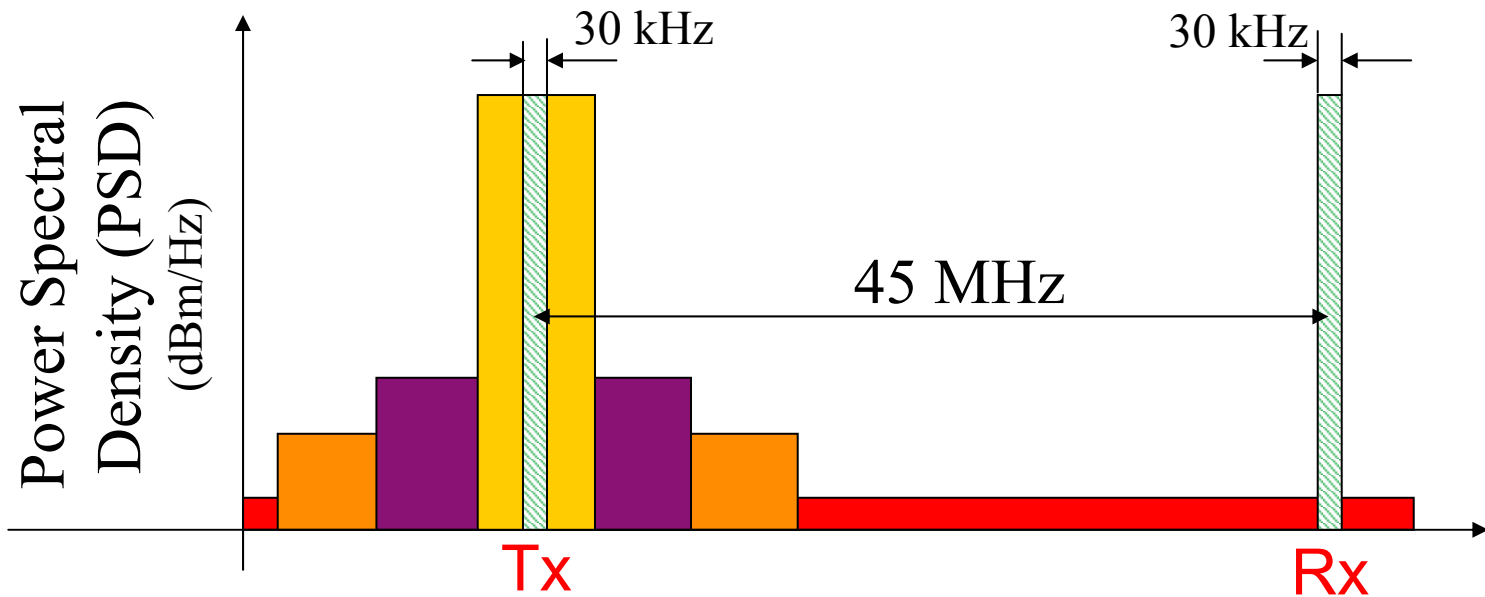
- Obvious spec. in systems where Tx and Rx are operating at the same time (FDD)






System Specifications

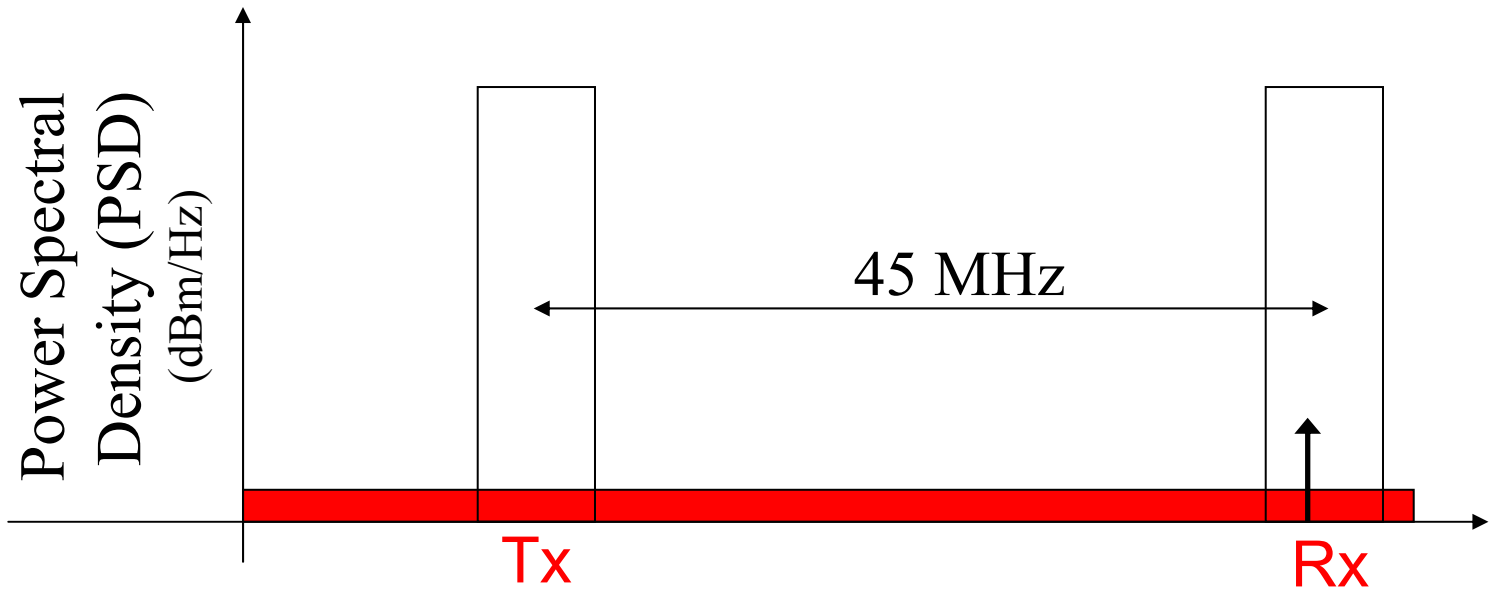- ◆ **Noise in receive band:**
 - Obvious spec. in systems where Tx and Rx are operating at the same time (FDD)
 - Not so obvious spec in TDD system. Problem primarily of mixing by the PA ($2\omega_2 - \omega_1$ or $\omega_2 - \omega_1$)



Power Control

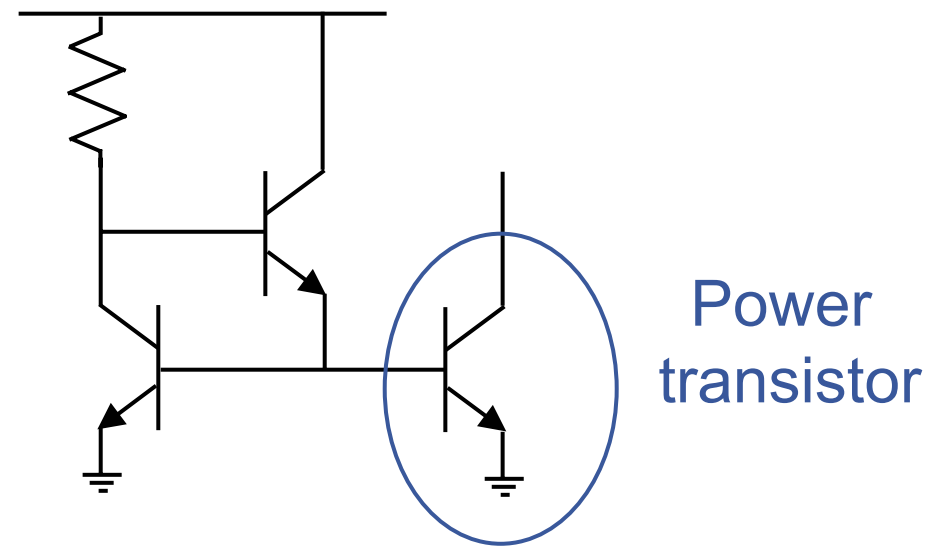- ◆ For linear PA, expected to operate at constant gain. Power control is therefore a function of P_{IN} .
- ◆ Role of bias circuitry is to maintain constant gain over P_{IN} , temperature (PTAT?).





Power Control

- ◆ For non-linear PA, expected to operate at constant P_{IN} . Power control is achieved by varying gain.

