

Class 12: Outline

Hour 1:

Working with Circuits

Expt. 4. Part I: Measuring V, I, R


Hour 2:

RC Circuits

Expt. 4. Part II: RC Circuits



Last Time: Resistors & Ohm's Law

Resistors & Ohm's Law

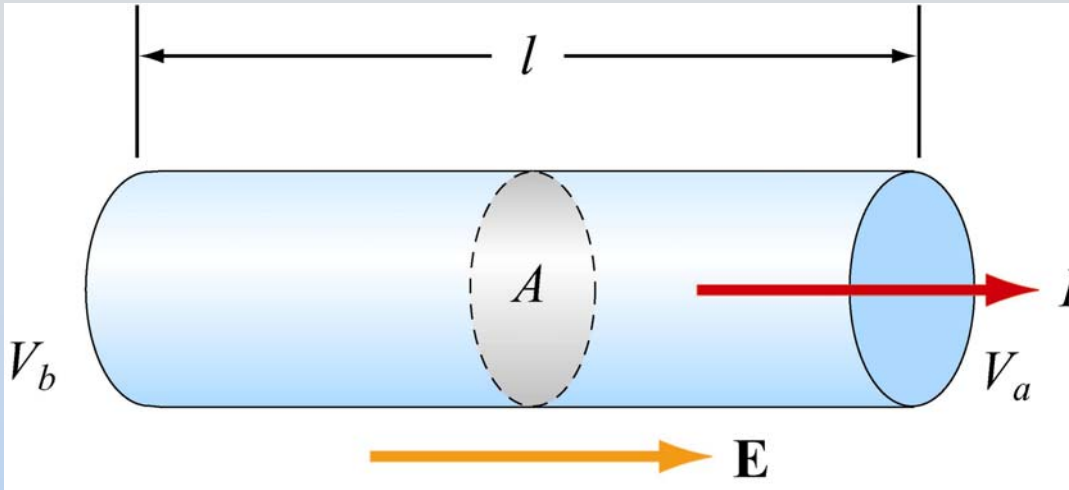

$$R = \frac{\rho l}{A}$$


$$\Delta V = IR$$

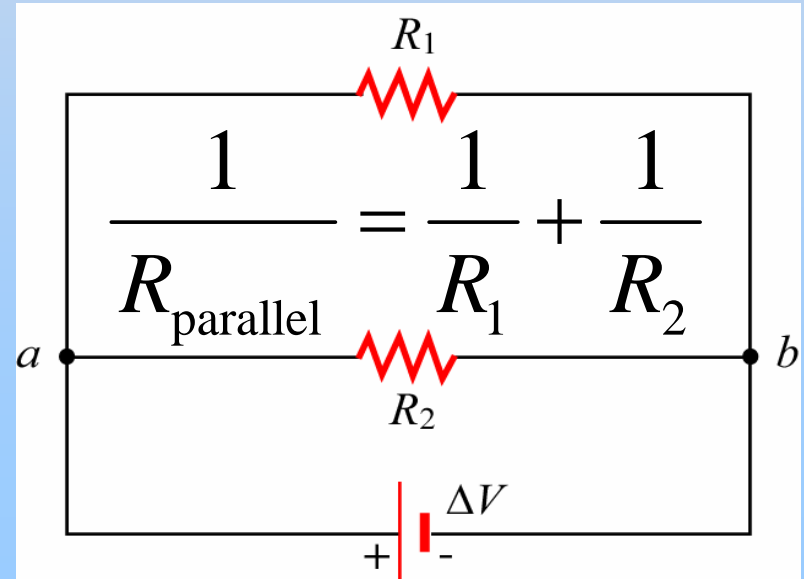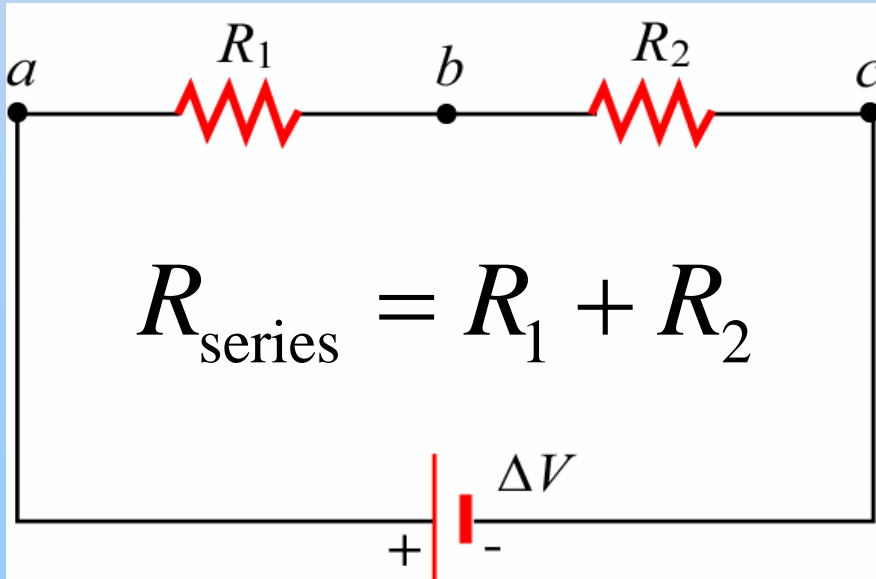

Measuring Voltage & Current

Measuring Potential Difference

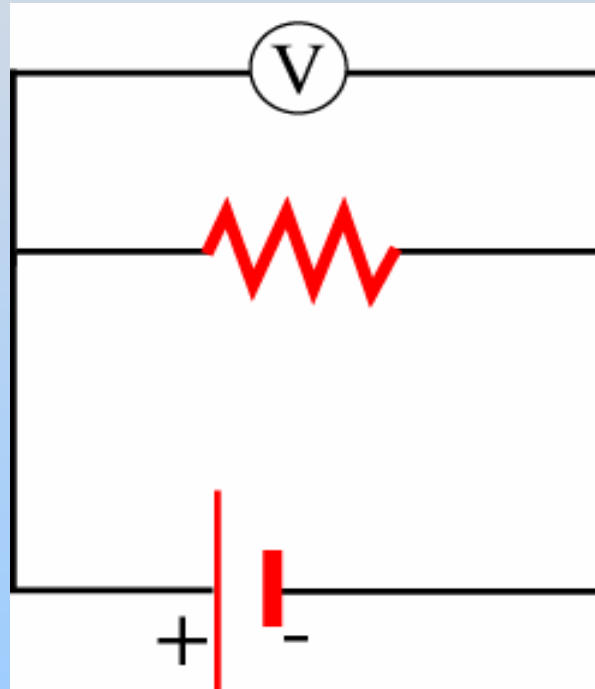
A voltmeter must be hooked in *parallel* across the element you want to measure the potential difference across



Voltmeters have a very large resistance, so that they don't affect the circuit too much

Measuring Current

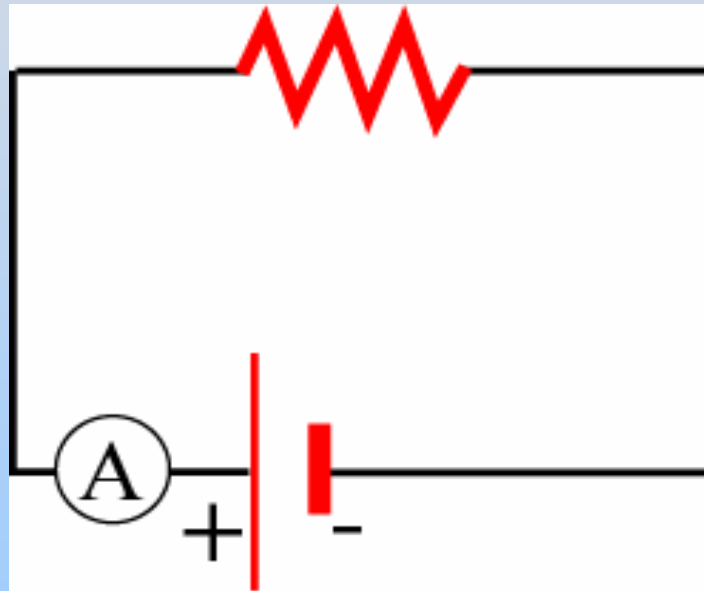
An ammeter must be hooked in *series* with the element you want to measure the current through



Ammeters have a very low resistance, so that they don't affect the circuit too much

Measuring Resistance

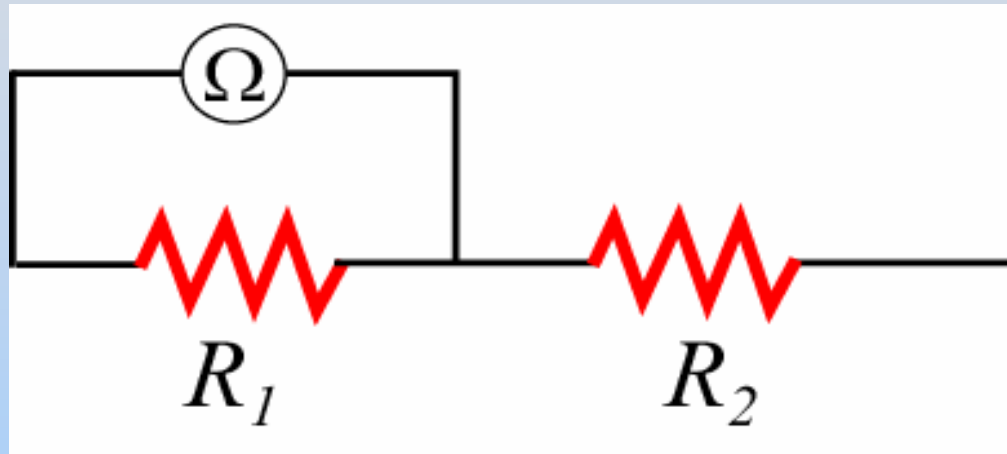An ohmmeter must be hooked in *parallel* across the element you want to measure the resistance of



Here we are measuring R_1

Ohmmeters apply a voltage and measure the current that flows. They typically won't work if the resistor is powered (connected to a battery)

Experiment 4:


Part 1: Measuring V, I & R

RC Circuits

(Dis)Charging a Capacitor


1. When the direction of current flow is toward the positive plate of a capacitor, then

$$I = + \frac{dQ}{dt}$$

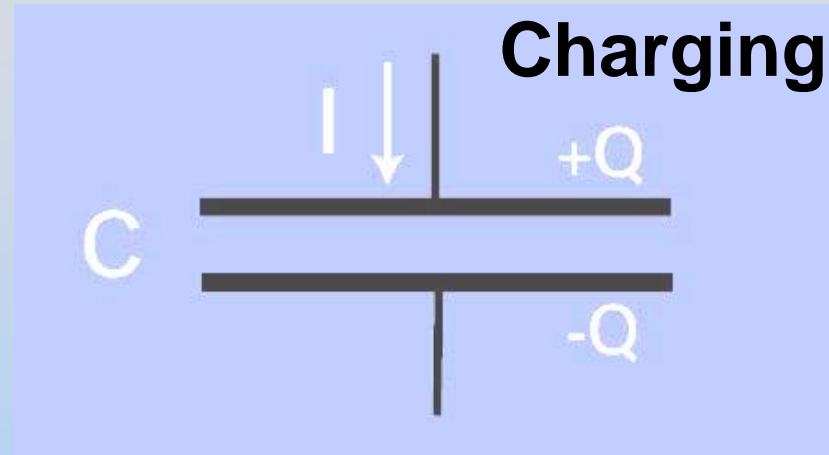


2. When the direction of current flow is away from the positive plate of a capacitor, then

$$I = - \frac{dQ}{dt}$$


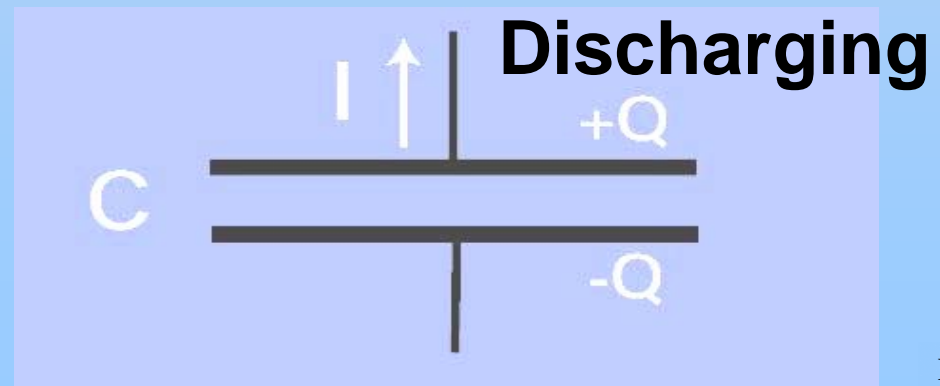


Charging A Capacitor

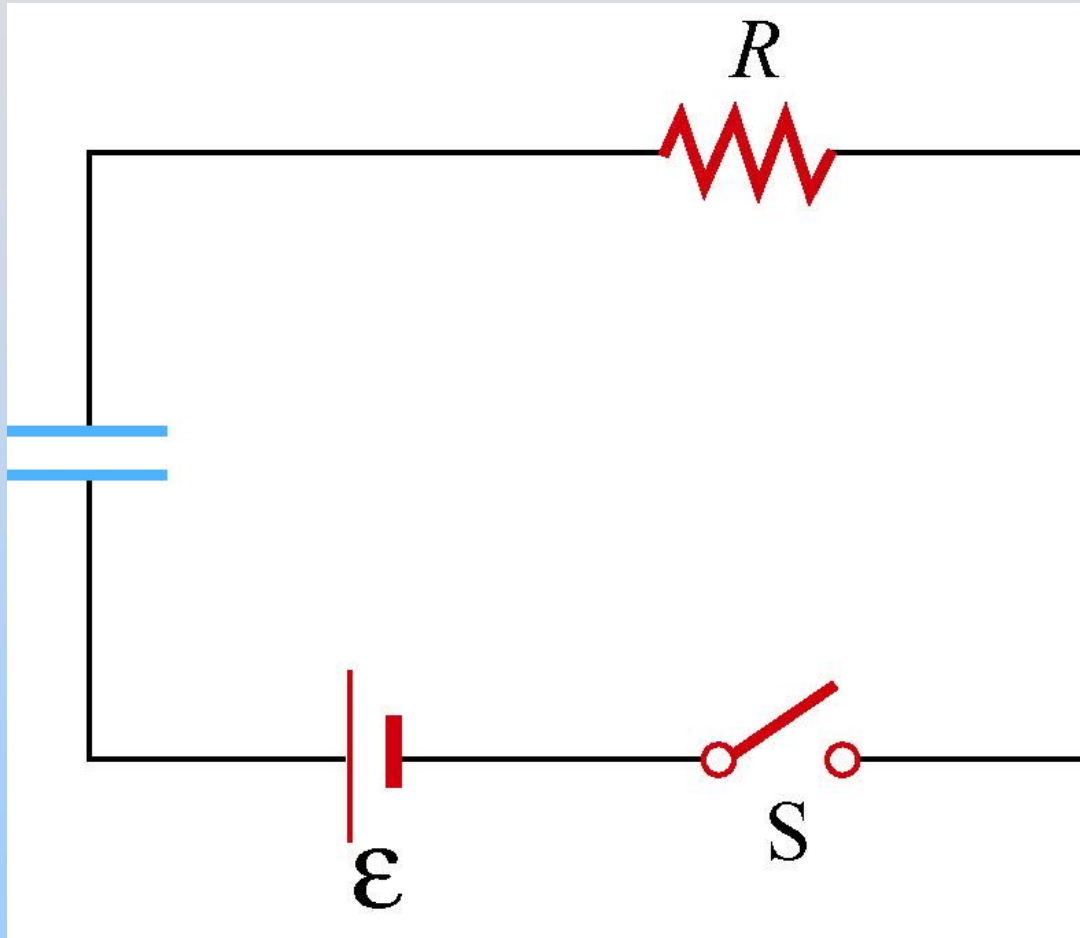

What happens when we close switch S ?


Charging A Capacitor

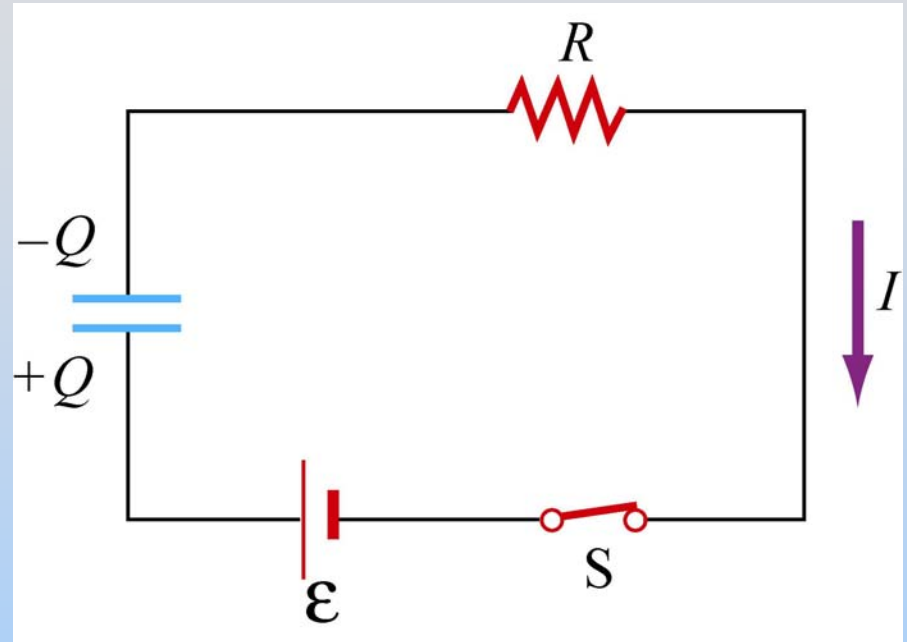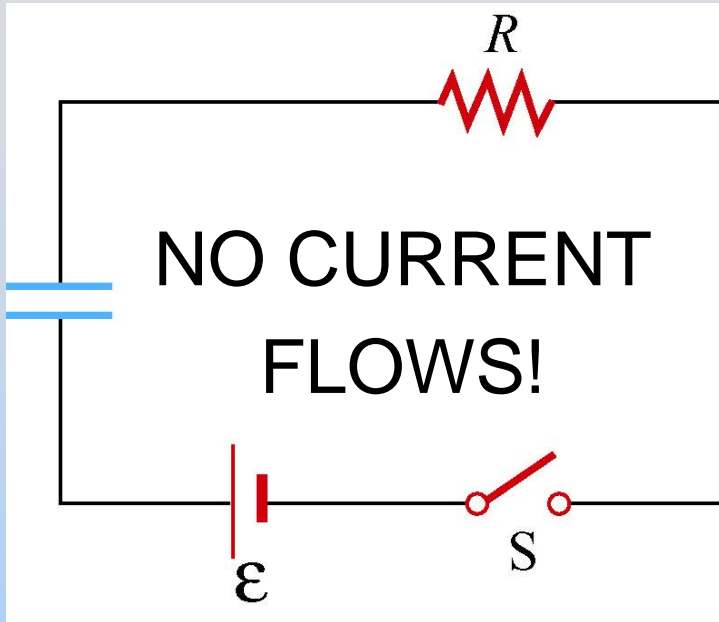

1. Arbitrarily assign direction of current
2. Kirchhoff (walk in direction of current):

$$\sum_i \Delta V_i = \varepsilon - \frac{Q}{C} - IR = 0$$

Charging A Capacitor

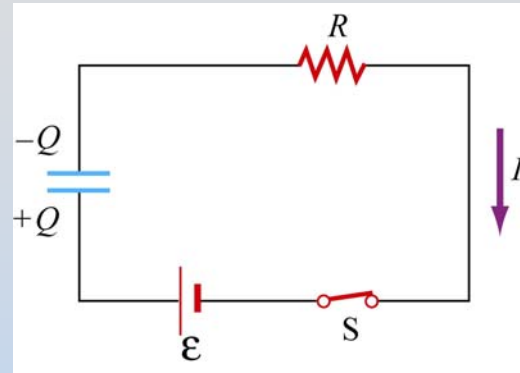

$$\mathcal{E} - \frac{Q}{C} = \frac{dQ}{dt} R \Rightarrow \frac{dQ}{Q - C\mathcal{E}} = -\frac{dt}{RC}$$


$$\int_0^Q \frac{dQ}{Q - C\mathcal{E}} = -\int_0^t \frac{dt}{RC}$$

A solution to this differential equation is:


$$Q(t) = C\mathcal{E} \left(1 - e^{-t/RC} \right)$$

RC is the time constant, and has units of seconds

Charging A Capacitor

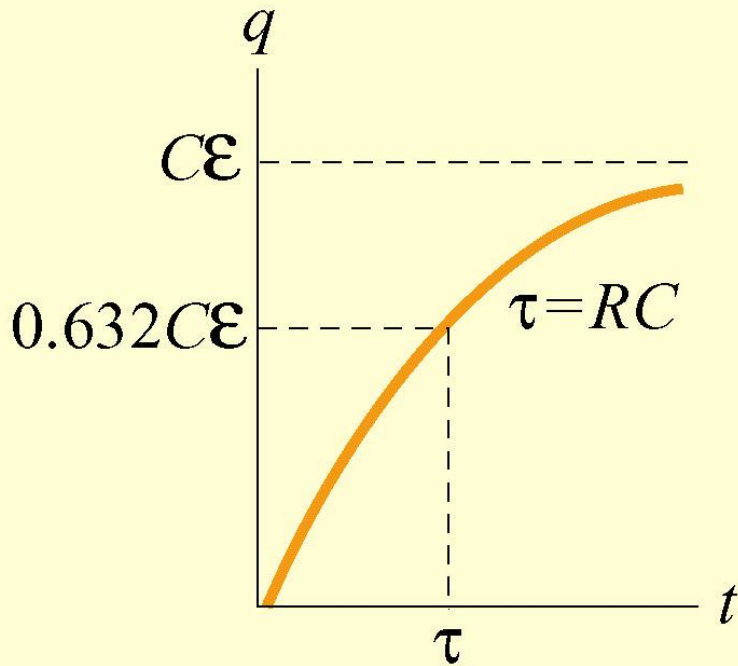

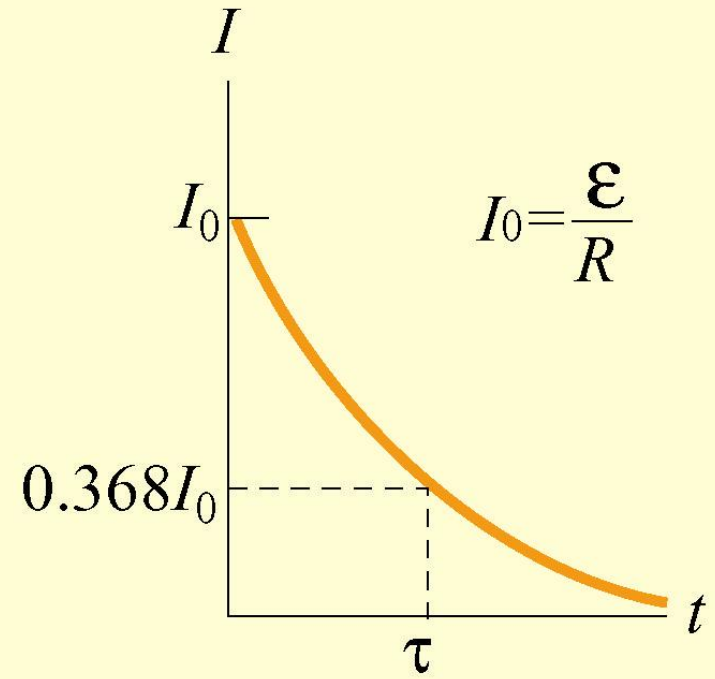
$$Q = C\mathcal{E} \left(1 - e^{-t/RC} \right)$$



$$I = \frac{dQ}{dt} = \frac{\mathcal{E}}{R} e^{-t/RC}$$



PRS Questions: Charging a Capacitor

Discharging A Capacitor

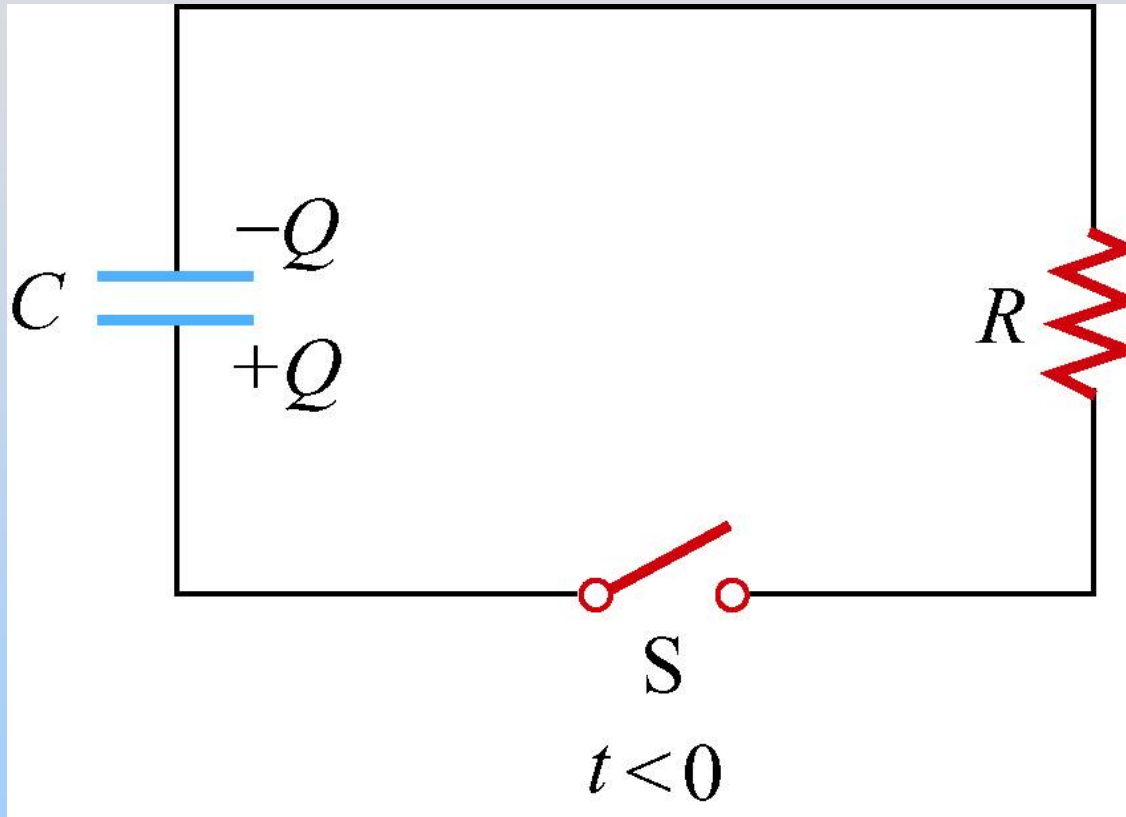

What happens when we close switch S ?

Discharging A Capacitor

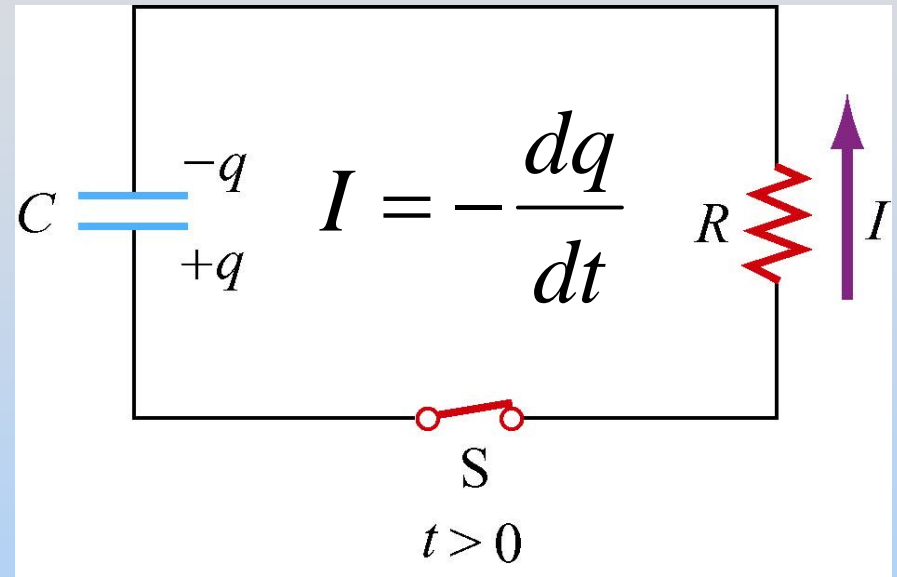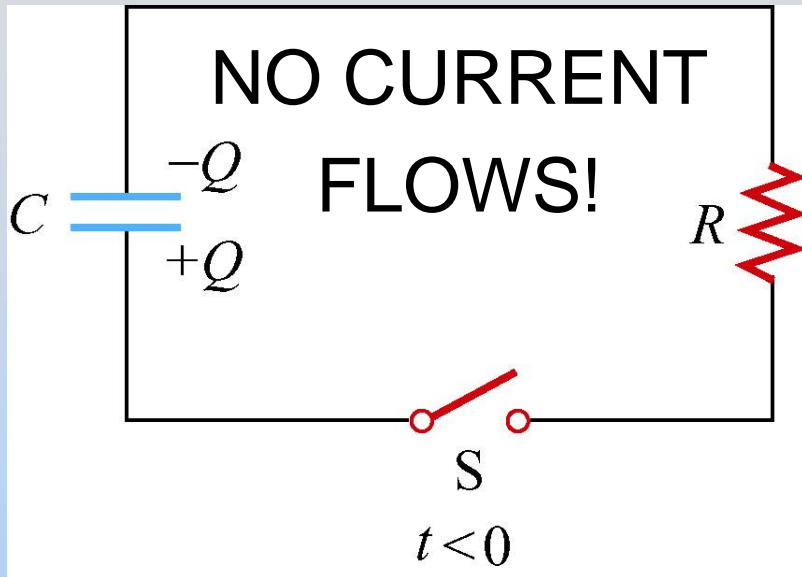


$$\sum_i \Delta V_i = \frac{q}{C} - IR = 0$$

Discharging A Capacitor


$$\frac{dq}{dt} + \frac{q}{RC} = 0 \Rightarrow \int_{Q_0}^Q \frac{dq}{q} = - \int_0^t \frac{dt}{RC}$$

$$Q(t) = Q_0 e^{-t/RC}$$

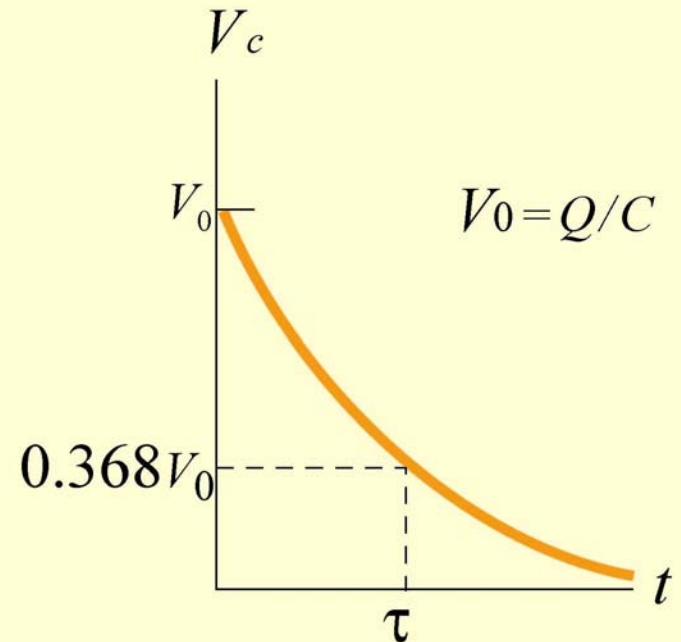


General Comment: RC

All Quantities Either:

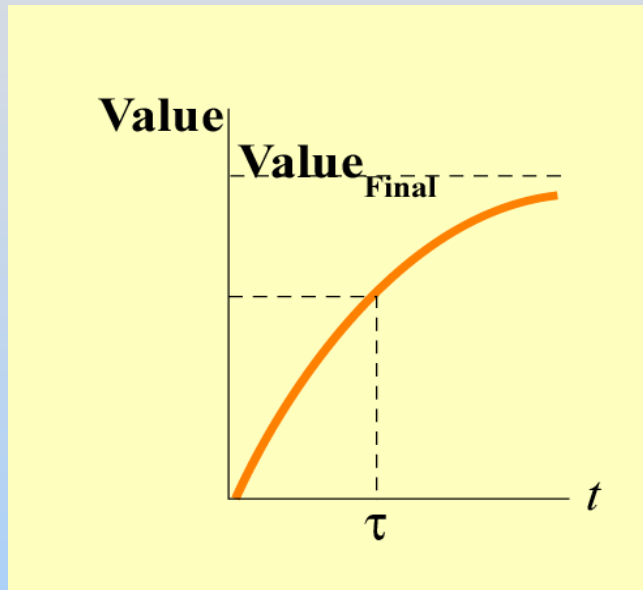

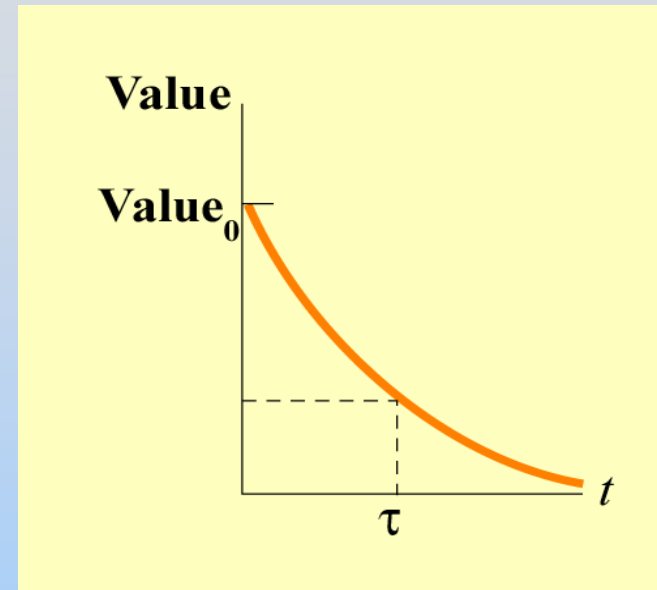
$$\text{Value}(t) = \text{Value}_{\text{Final}} \left(1 - e^{-t/\tau}\right)$$



$$\text{Value}(t) = \text{Value}_0 e^{-t/\tau}$$

τ can be obtained from differential equation
(prefactor on d/dt) e.g. $\tau = RC$

Exponential Decay

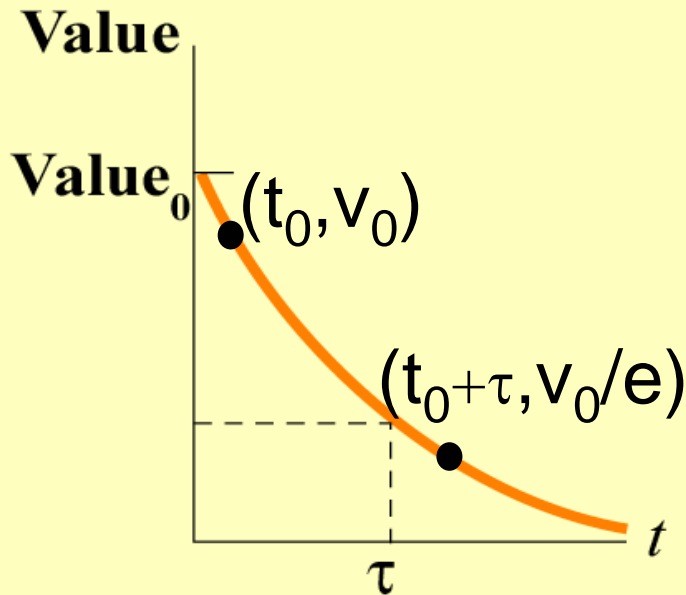

$$\text{Value}(t) = \text{Value}_0 e^{-t/\tau}$$

Very common curve in physics/nature

How do you measure τ ?

- 1) Fit curve (make sure you exclude data at both ends)
- 2) a) Pick a point
b) Find point with y value down by e
c) Time difference is τ

Demonstrations: RC Time Constants

Experiment 4:

Part II: RC Circuits

**PRS Question:
Multiloop circuit with Capacitor
in One Loop**